

→ TRANSFORMERS:

General representation:- Rated KVA, E_1/E_2

$$E_1 \approx V_1, E_2 \approx V_2.$$

$$E_1 = 4.44 \times f \times \phi_m \times N_1 = 4.44 \times f \times B_m \times A \times N_1$$

$$E_2 = 4.44 \times f \times \phi_m \times N_2 = 4.44 \times f \times B_m \times A \times N_2.$$

$$K: \frac{E_2}{E_1} = \frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} \quad (\text{Transformation ratio})$$

$K > 1 \rightarrow$ Step up, $K < 1 \rightarrow$ Step down, $K = 1 \rightarrow$ Isolation.

For any trans:- $V_1 I_1 : V_2 I_2$.

$$\text{If full load: } \frac{I_1 \text{ full load}}{V_1} = \frac{\text{KVA rating} \times 1000}{V_1}, \quad \frac{I_2 \text{ full load}}{V_2} = \frac{\text{KVA rating} \times 1000}{V_2}$$

Actual VA = \times Rated VA (full load)

\downarrow primary winding resist \downarrow secondary reactance \downarrow leakage reactance

$$R_{01} = R_1 + \frac{R_2}{K^2}, \quad X_{01} = \frac{X_1 + X_2}{K^2}, \quad R'_2 = \frac{R_2}{K^2}, \quad X'_2 = \frac{X_2}{K^2}$$

Eq resist referred to primary
Component is referred from secondary to primary value
divide by K^2

Component from primary \rightarrow secondary multiply by K^2

$$R_{02} = K^2 R_{01}, \quad X_{02} = K^2 X_{01}$$

$$\text{Efficiency: } \eta = \frac{V_2 I_2 \cos \phi}{V_2 I_2 \cos \phi + W_i + W_{cu}} \times 100.$$

$$\eta = \frac{x \text{ Rated KVA} \times \cos \phi}{x \text{ Rated VA} \cos \phi + W_i + x^2 W_{cu} f} \times 100.$$

$$W_{cu} = I_1^2 R_{01}$$

$$= x^2 I_1^2 F \cdot R_{01}$$

$$W_{cu} = x^2 W_{cu} F.$$

For η_{max} :- $W_i = W_{cu}$

$$W_i = \frac{V_1^2}{X^2} W_{cuFL}$$

Load VA (η_{max}) : Full load VA $\times \frac{W_i}{W_{cuFL}} = V_2$

$$\text{Load VA } (\eta_{max}) = V_2 I_2 \frac{W_i}{W_{cuFL}}$$

→ Voltage regulation:

$$\begin{aligned} 1. V \cdot R &= I_1 (R_0 \cos \phi \pm X_0 \sin \phi) \\ &= I_2 (R_0 \cos \phi \pm X_0 \sin \phi) \end{aligned}$$

Inductive load :- + lag p.f.
Capacitive load :- - lead p.f.

→ O.C. And S.C. Test (If low-volt side is shorted, means test on high-voltage side)

O.C. test on primary:

$$V_1, W_i, I_0$$

$$1. \phi_0 = \cos^{-1} \left(\frac{W_i}{V_1 I_0} \right)$$

$$2. I_w = I_0 \cos \phi_0 \quad \text{or} \quad R_o$$

$$3. I_u = I_0 \sin \phi_0$$

$$4. R_o = \frac{V_1}{I_w}$$

$$5. X_0 = \frac{V_1}{I_u}$$

O.C. test on secondary

$$V_{sc}, I_{sc}, W_{sc}, V_2, I_0', W_i$$

$$1. R_{o2} = \frac{W_{sc}}{I_{sc}} \quad \phi_0 = \cos^{-1} \left(\frac{W_i}{E_2 I_0} \right)$$

$$2. I'_w = I_0' \cos \phi_0$$

$$3. I'_u = I_0' \sin \phi_0$$

$$4. R_o = \frac{E_2}{I'_w} \quad \therefore R_o = \frac{R_o}{K^2}$$

$$5. X'_0 = \frac{E_2}{I'_u} \quad \therefore X_0 = \frac{X_0}{K^2}$$

S.C. test on primary

$$V_{sc}, I_{sc}, W_{sc}$$

$$1. R_{o1} = \frac{W_{sc}}{I_{sc}^2}$$

$$2. Z_{o1} = \frac{V_{sc}}{I_{sc}}, \quad 3. X_{o1} = \sqrt{Z_{o1}^2 - R_{o1}^2}$$


S.C. test on secondary

$$V_{sc}, I_{sc}, W_{sc}$$


$$1. R_{o2} = \frac{W_{sc}}{I_{sc}^2}$$

$$2. Z_{o2} = \frac{V_{sc}}{I_{sc}}, \quad 3. X_{o2} = \sqrt{Z_{o2}^2 - R_{o2}^2}$$

Premary:-

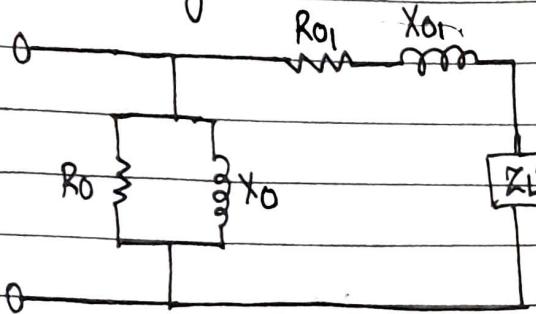

Secondary:-

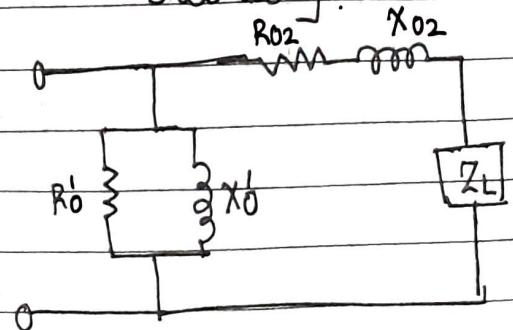

→ EMF Eqn:

$$\text{Avg rate of change of } \phi : \frac{\phi_m - 0}{T/4 - 0} = \frac{4\phi_m}{T}$$

Variation is same in each quarter cycle:-

For Sine wave,

$$K_f = \text{RMS} = 1.11 \\ \text{Avg}$$



$$\text{RMS rate of change of flux} : 1.11 \times \frac{4\phi_m}{T} = 4.44 \frac{\phi_m}{T} = 4.44 f \phi m$$

Acc to Lenz's law. EMF induced per turn : $\frac{d\phi}{dt} = 4.44 f \phi m$

$$E_1 = 4.44 f \phi m N_1, E_2 = 4.44 f \phi m N_2.$$


→ Ideal, no load.

→ Practical, no load

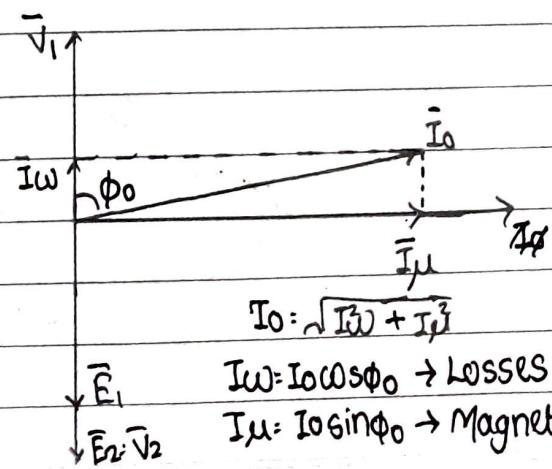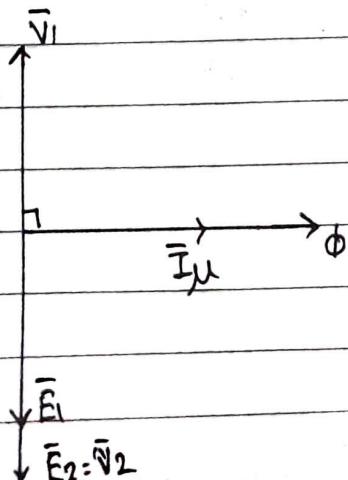


→ Resistive: Capacitor

→ Inductive

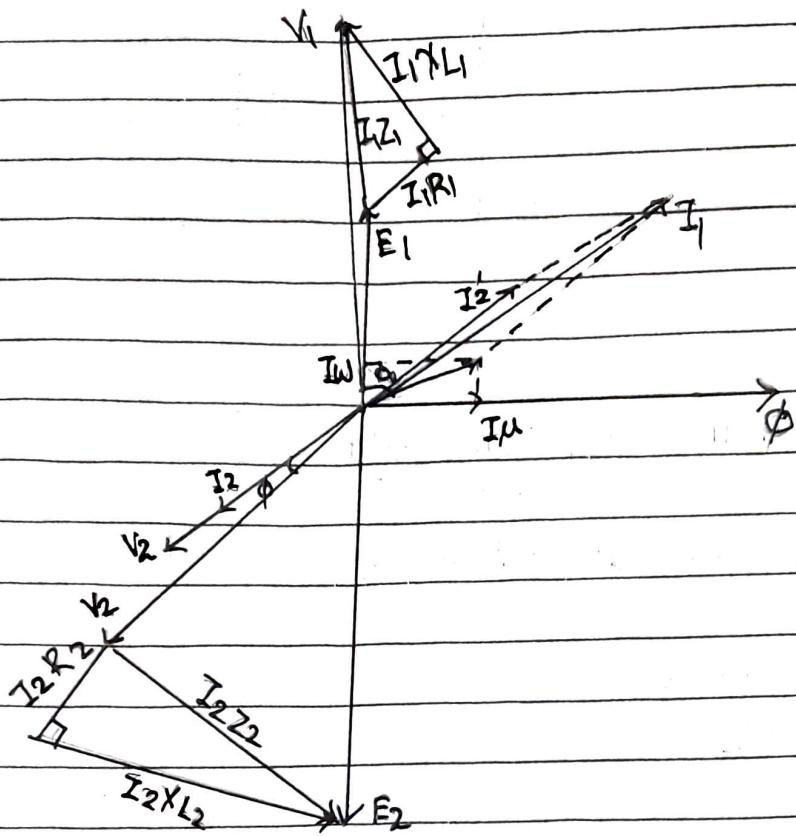


→ Capacitive

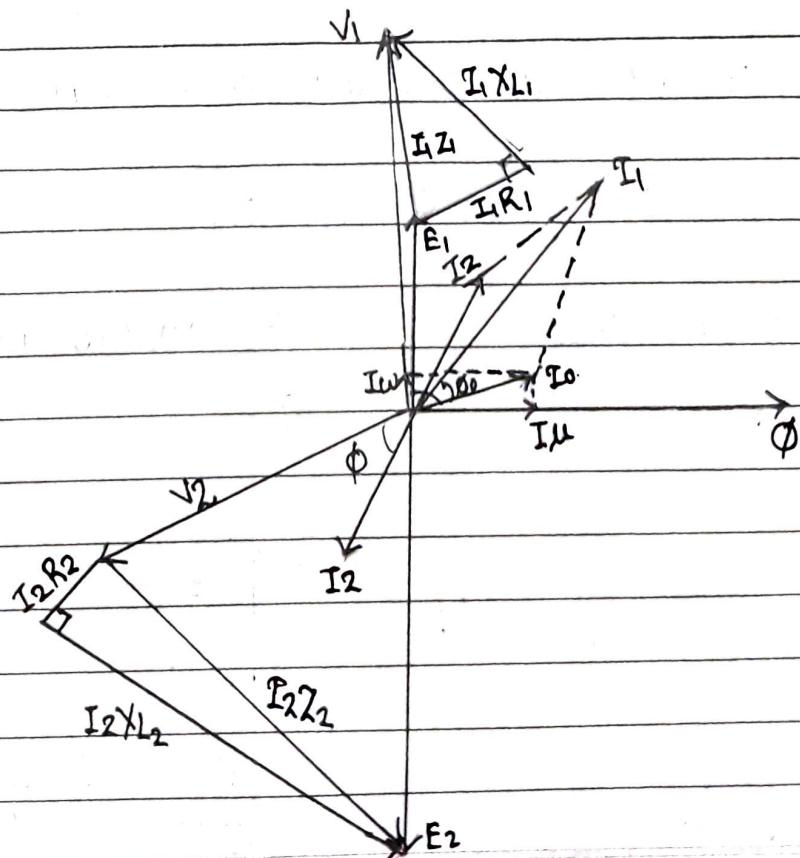

→ POWER CONVERTORS

1. Buck:-

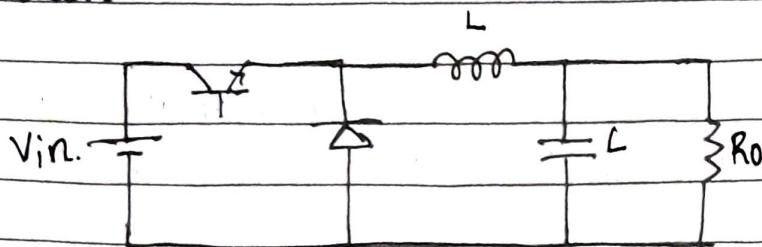


$$V_o = V_{in} \cdot d \quad L = \frac{\Delta i_L}{8f_s \cdot \Delta V} \quad L = \frac{V_o (1-d)}{\Delta i_L \cdot f_s} \quad L = \frac{\Delta i_L \times f_s \times V_{in(\max)}}{V_{out}}$$

For $d_{\min} \rightarrow V_{in \max}$ & vice-versa.

$$\Delta i_L = 0.1 \times I_{out}, \quad \Delta V = 2\% \cdot V_{out} \Rightarrow 0.2 \times V_{out}$$


2. Boost:-

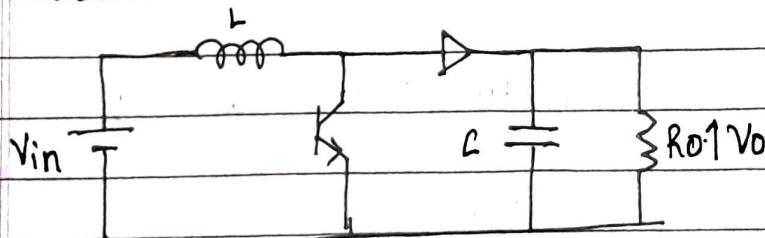

$$V_o = \frac{V_{in}}{1-d}, \quad L = \frac{I_o \cdot d}{\Delta V \cdot f_s} \quad L = \frac{V_{in} \cdot d}{\Delta i_L \cdot f_s} \quad L = \frac{V_{in} \times (V_{out} - V_{in})}{\Delta i_L \times f_s \times V_{out}}$$

$$\Delta i_L = 0.1 \times I_{out}, \quad \Delta V = 2\% \cdot V_{out} = 0.2 \times V_{out}$$

3. Buck-Boost:-

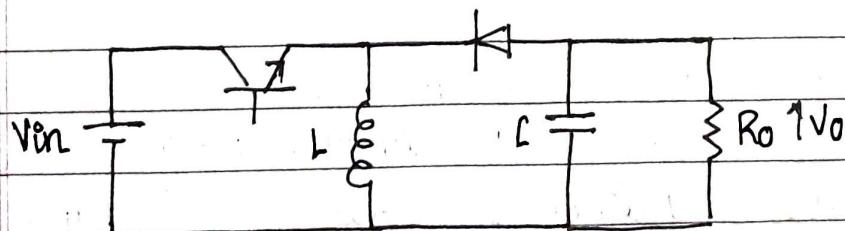

$$V_o = -V_{in} \cdot \frac{d}{1-d}, \quad L = \frac{I_o \cdot d}{\Delta V \cdot f_s} \quad L = \frac{V_{in} \cdot d}{\Delta i_L \cdot f_s} = \frac{V_{in(\max)} \times D_{\min}}{\Delta i_L \times f_s}$$

$$D_{\min} = \frac{V_o}{V_o + V_{in(\max)}}, \quad I_{\max} = \frac{V_o}{V_{in(\min)} + V_o}, \quad \Delta i_L = 0.1 \times I_{out}, \quad \Delta V = 0.2 \times V_{out}$$

→ DC MACHINES

$$1. E_b = \frac{\phi Z N P}{60A}$$


E_b : Back emf, ϕ : Flux/pole, Z : Total no. of armature conductor

N : Speed of armature in RPM, P : no. of poles, A : no. of parallel paths

$$2. \text{ Voltage eqn: } V = E_b + I_a R_a - \text{Motor.} \quad V = E_b - I_a R_a - \text{Generator}$$

$$V_{ia} = E_b I_a + I_a^2 R_a$$

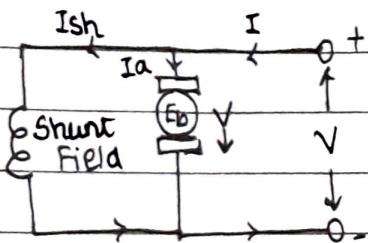Input to armature \Rightarrow mech power \rightarrow loss in armature.



$$3. \text{ Torque: } P = \frac{2\pi N}{60} \times T, \text{ Armature torque: } T_a = 0.159 \cdot \phi \cdot Z \cdot I_a \times \left(\frac{P}{a}\right)$$

$$4. \text{ Torque shaft: } T_{sh} = \frac{0.55 \cdot \text{Output}}{N} \cdot \text{N-m}$$


$$5. \frac{N_2}{N_1} = \frac{E_{b2} \times I_{a1}}{E_{b1} \times I_{a2}} \dots \text{Suffix 1,2 (1st case, 2nd case)} \quad \phi \propto I_a \\ (\text{Series motor})$$

$$\frac{N_2}{N_1} = \frac{E_{b2} \times \phi_1}{E_{b1} \times \phi_2} \quad (\text{Shunt motor})$$

$$6. N = K \left(\frac{V - I_a R_a}{\phi} \right) \quad T_a \propto \phi I_a$$


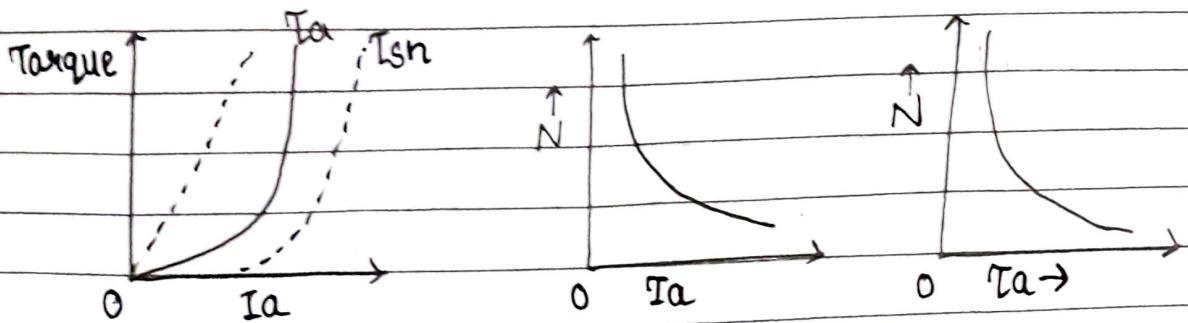
7. Series motor: Variable speed motor.

Used in places where huge starting torque is reqd.
acc. heavy masses, quickly in hoists & electric fan.



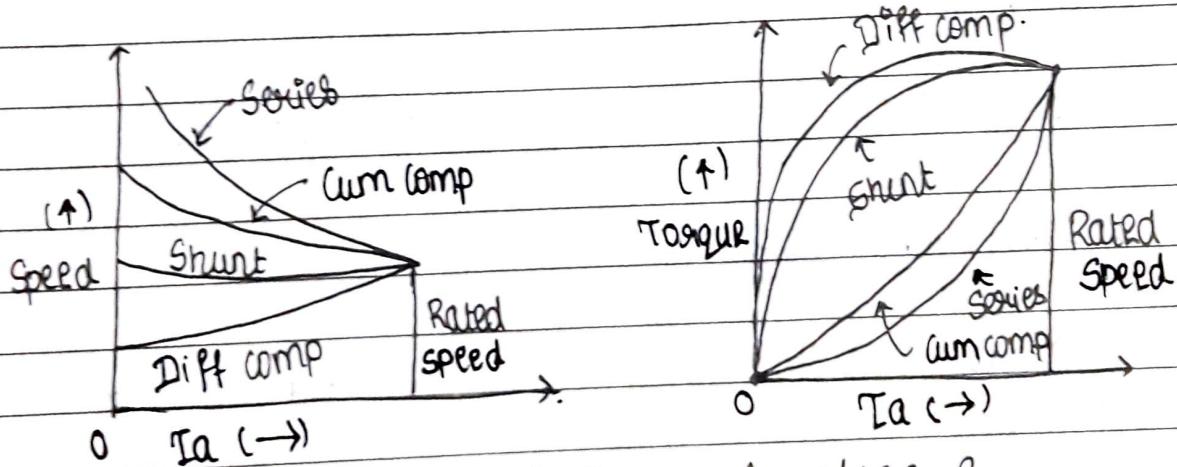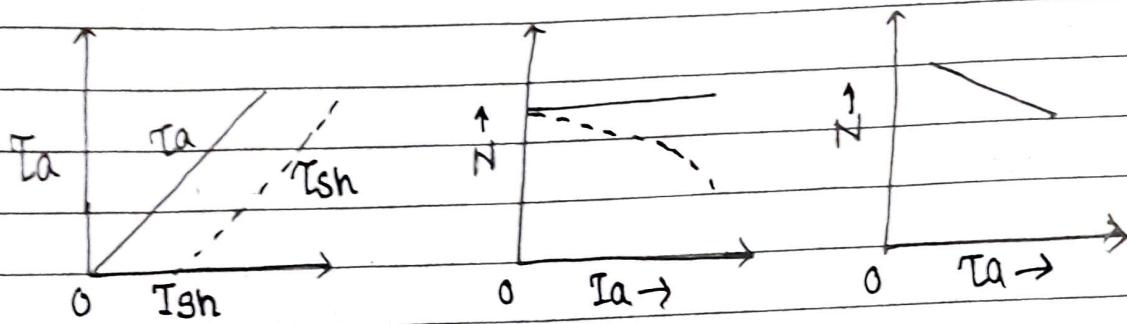
8. Shunt Motor: Const speed motor

Heavy starting torque needed \therefore should not be used at heavy load



* lap winding = $\frac{1}{2}$ path - Poles, Armature = 2


i) Series wound:

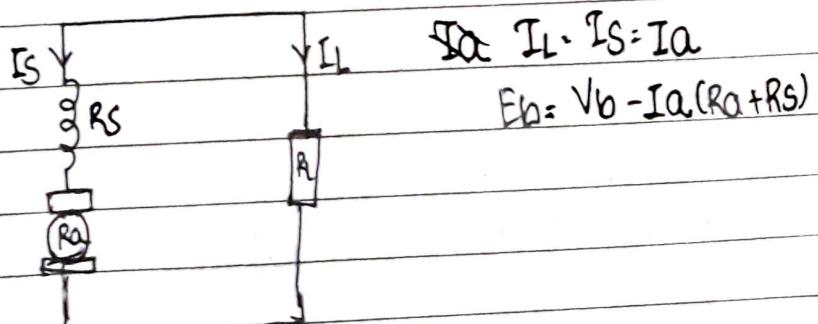

$$I_L \cdot I_S = I_a$$

$$E_b = V_b - I_a(R_a + R_s)$$

ii) Shunt Motor:

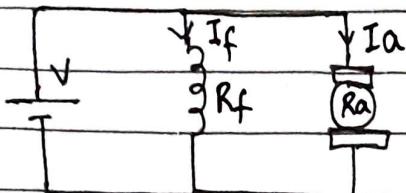


$$I_f = \frac{V}{R_f}$$

$$I_a = I_L + I_f$$

$$E_b = V - I_a R_a$$

iii) Shunt Shunt

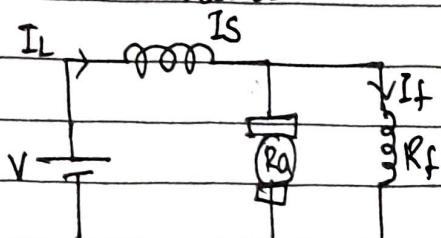


$$I_s = I_L$$

$$I_b = V - I_a R_a - I_s R_s$$

$$I_a = I_L + I_f$$

$$E_f = V - \frac{I_L R_s}{R_s}$$

Long Shunt

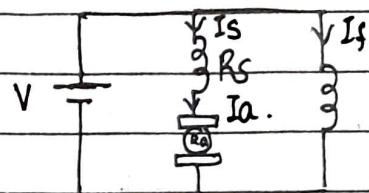

$$I_a = I_s = I_L + I_f$$

$$I_f = \frac{V}{R_f}$$

$$E_b = V - I_a (R_a + R_s)$$

→ INDUCTION MOTOR

1. P: $2n$, n = no. of stator/pole

2. Synchronous speed: $N_s = 120 \cdot f_p$

3. % Slip (s): $N_s - N / N_s \times 100$, $N_s - N = 120f_s$

4. $120f_s = 120f_p = sN_s$. . . $s = f_s / f$

5. Speed: $N = N_s(s-1)$

6. Starting torque: $T_{st} = \frac{K_1 E_2^2 R_2}{R_2^2 + X_2^2}$

7. Running torque:

$$T = \frac{3}{2} \cdot \frac{SE_2^2 R_2}{2\pi N_s} T_{max}$$

$$R_2 = S X_2$$

8. Breakdown torque:

$$T = T_s \left[\frac{2}{\left(\frac{S_b}{S} \right) + \left(\frac{S}{S_b} \right)} \right]$$

$$= \frac{3}{2\pi N_s} \cdot \frac{E_2^2 R_2}{R_2^2 + X_2^2}$$

$$T_{max}: X_2 = R_2$$

→ MAGNETIC CIRCUITS

$$1. H = \frac{mmf}{\text{length}} = \frac{IN}{l}$$

2. Reluctance:

$$R = \frac{l}{\mu_0 A} = \frac{1}{\mu_0 A} l = \frac{F}{\Phi}$$

$$H = \frac{F}{l} \Rightarrow \frac{\Phi}{l} = \frac{BA}{l} = \frac{\mu_0 A}{l} \cdot \frac{N}{l} = \frac{N \mu_0 A}{l^2}$$

$$R = \frac{l}{\mu_0 A} \Rightarrow \frac{1}{R} = \frac{\mu_0 A}{l}$$

3. Kirchoff's Flux Law: At a particular junⁿ.

$$\phi_L = \phi_m + \phi_N$$

Kirchoff's magnetomotive law:

The algebraic sum of the product of the field strength & length of each part of the ckt is equal to resultant mmf

$$\text{Total mmf} = H_1 l_1 + H_m l_m + H_n l_n = 0$$

4. Self inductance: $e \propto \frac{di}{dt} \quad L = L \cdot \frac{di}{dt}$

$$L = N \cdot \frac{d\phi}{dt} \quad \text{For linear,}$$

$$\phi = \frac{Ni}{R} \quad \& \quad L = \frac{N^2 \mu A}{l}$$

5. Mutual inductance: $M_{12} = N_2 \cdot \frac{d\phi_{12}}{dt}, \quad M_{21} = N_1 \cdot \frac{d\phi_{21}}{dt}$

~~$M_{12} = N_1 M_{21}$~~

6. Coeff coupling : $K = \frac{M}{\sqrt{L_1 L_2}}$

7. flux aid: $V = (L_1 + L_2 + 2M) \frac{di}{dt}$
flux oppos: $V = (L_1 + L_2 - 2M) \frac{di}{dt}$

→ BATTERIES

1. Battery capacity: $E = \int_0^t (V_b \cdot i_b) dt$

2. Charge capacity: $Q = \int_0^t i_n dt$

3. DOD (Depth of discharge)(y) is a % measure of how much battery is empty with ref to its nominal charge capacity.
 SOC (State of charge) is a % how much battery is filled with ref to its nominal charge capacity.
 If $x: 100-y$ then $y: 100-x \rightarrow$ complementary.

4. C-rate is defined as the rate at which charge cap of battery reqd to charge or discharge

$$I_b = \frac{C}{N}, \text{ e.g. } C_1 \geq 100A \text{ in 1hr} \quad \text{If } I_b = 5A, \text{ for } N=20 \Rightarrow C_{20}$$

$$C_{10} \geq 100A \text{ in 10hr}$$

$$I_b = 200A \text{ for } N=0.5, \left(\frac{C}{0.5}\right) 2C$$

$$I_b = 20A \text{ for } N=5, C_5$$

5. Battery efficiency:

$Wh_{SC} \neq$ net energy drawn from source charging = electrical \rightarrow chem.

Wh_{EC} = energy loss during charging.

Wh_{DC} = energy loss during discharging discharging = chem \rightarrow electrical

$$\eta = \frac{Wh_{SC}}{Wh_{SC} + (Wh_{EC} + Wh_{DC})} \times 100$$

6. Battery selections:

a) App. availability, capital

b) Selection of C-rating

b) Allowable DOD

i) Average Id.

c) Wh requirement, Am

ii) low discharge current \rightarrow st line

d) Ampera rating

id.t.

$$Wh_{batt} = \frac{Wh_{load}}{DOD}, Ah_{batt} = \frac{Wh_{batt}}{V_{nom}}$$

iii) High discharge \rightarrow parabola
id.t.


→ DC TRANSIENTS

1. Inductor:


$$t=0^-$$



$$t=0^+$$

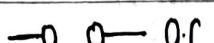

$$t=\infty$$

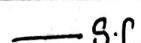

$$\rightarrow \text{---} \overset{I_0}{\text{---}}$$

$$\overset{I_0}{\text{---}} \text{---} \text{---}$$

$$\text{---} \text{---} \text{---} \overset{I_0}{\text{---}}$$

2. Capacitor:

$$t=0$$

$$\text{---} \text{---}$$

$$t=0^+$$

$$\text{---} \text{---}$$

$$t=\infty$$

$$\text{---} \text{---} \text{---}$$

$$\text{---} \text{---} \overset{V_0}{\text{---}}$$

$$\text{---} \text{---} \overset{V_0}{\text{---}}$$


$$\text{---} \text{---} \text{---} \overset{0}{\text{---}}$$


4. $T_0 = \frac{L_{eq}}{R_{eq}}$, $T = R_{eq} \times L_{eq}$.

5. $\frac{di}{dt} + Pi = Q$. $i(t) = e^{-Pt} \int Q e^{Pt} dt + R e^{-Pt}$.

→ 3-PHASE AC CIRCUITS

1. Star connection:

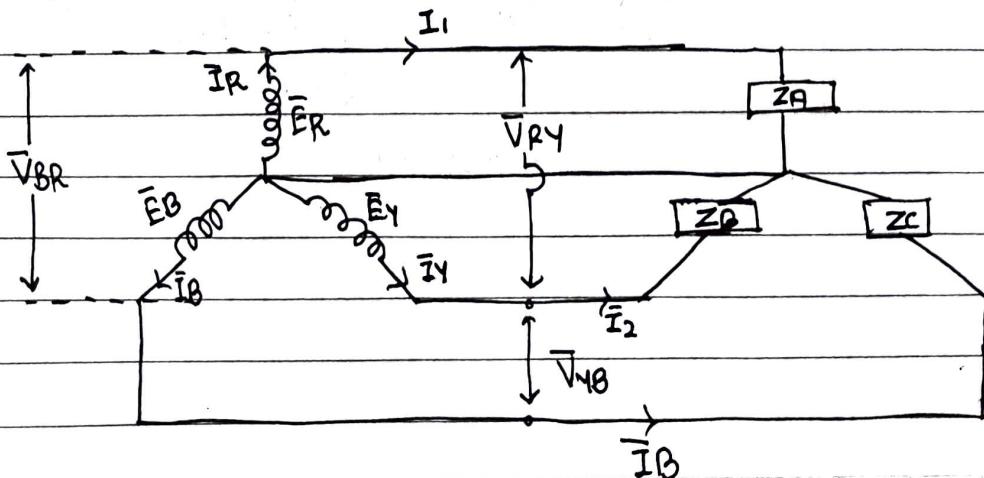

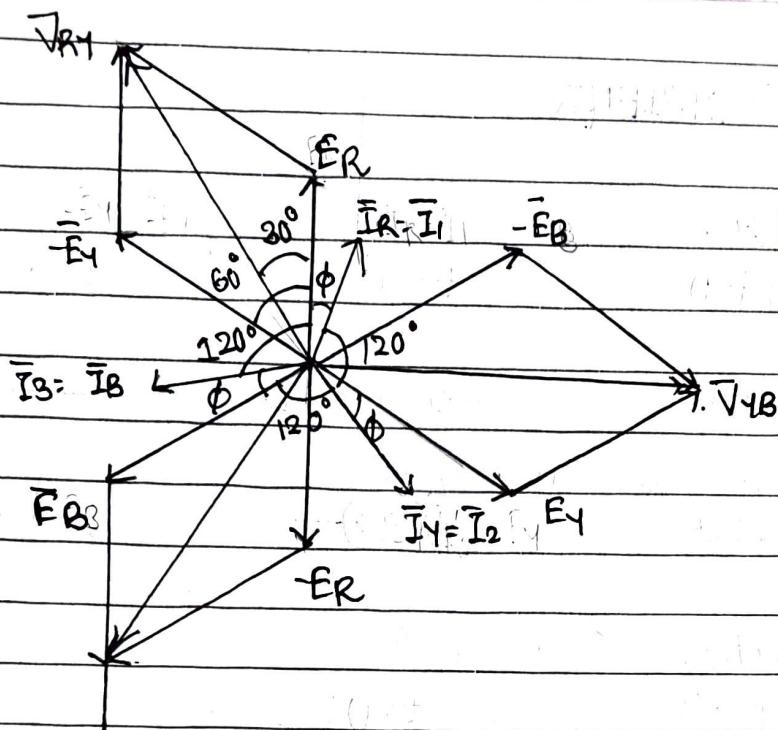

$$\bar{I}_R = \bar{I}_Y + \bar{I}_B, \quad \bar{I}_Y = \bar{I}_B, \quad \therefore \bar{I}_R = \bar{I}_B : \bar{I}_R = I_{ph}$$


$$\bar{V}_{RY} = \bar{E}_R - \bar{E}_Y, \quad \bar{V}_{YB} = \bar{E}_Y - \bar{E}_B \quad \& \quad \bar{V}_{BR} = \bar{E}_B - \bar{E}_R$$


$$V_{RY}^2 = \bar{E}_R^2 + \bar{E}_Y^2 + 2\bar{E}_R\bar{E}_Y \cos 60^\circ$$

$$V_L^2 = E_{ph}^2 + I_{ph}^2 + 2E_{ph}I_{ph} \times \frac{1}{2} = 3E_{ph}^2$$

$$V_L = \sqrt{3}E_{ph}, \quad \therefore E_{ph} = \frac{V_L}{\sqrt{3}} \quad \& \quad V_L \text{ leads } E_{ph} \text{ by } 30^\circ$$

2. Row or Delta connection.

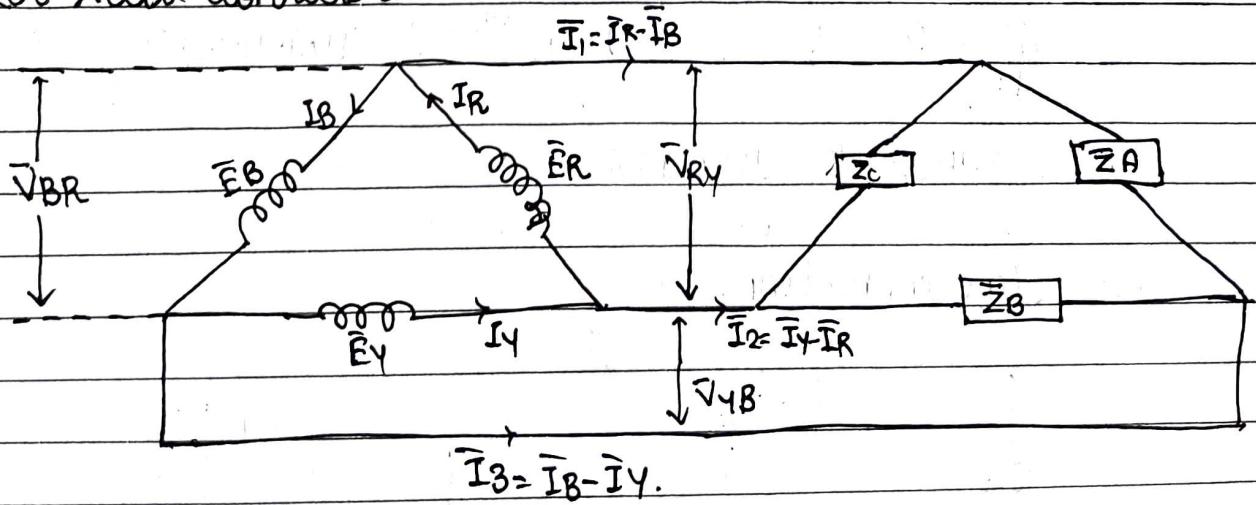

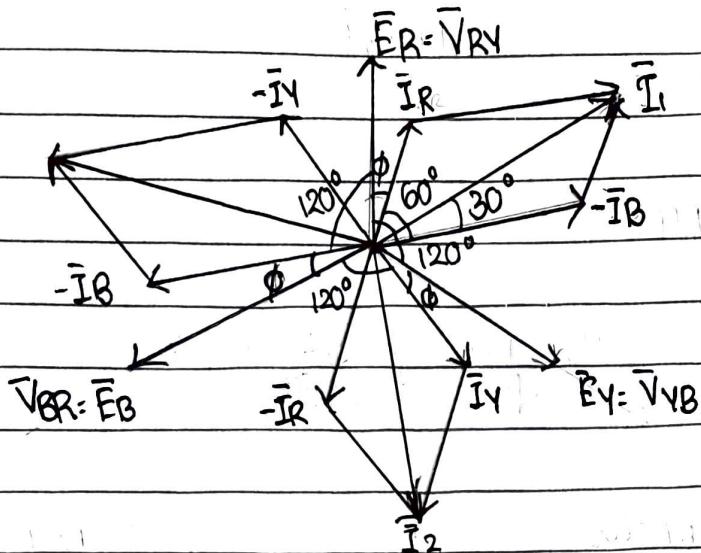

$$\bar{E}_R = \bar{V}_{RY}, \bar{E}_Y = \bar{V}_{YB}, \bar{E}_B = \bar{V}_{BR}, E_{ph} = V_L.$$

$$\bar{I}_1 = \bar{I}_R - \bar{I}_B, \quad \bar{I}_2 = \bar{I}_Y - \bar{I}_R, \quad \bar{I}_3 = \bar{I}_B - \bar{I}_Y$$

$$I_L^2 = I_R^2 + I_B^2 + 2I_R \cdot I_B \cdot \cos 60^\circ$$

$$I_L^2 = I_{ph}^2 + I_{ph}^2 + 2(I_{ph})(\frac{1}{2}) = 3I_{ph}^2$$

$$I_L = \sqrt{3} I_{ph} \text{ or } I_{ph} = I_L / \sqrt{3}, I_L \text{ lags by } 30^\circ$$

$$\text{Power: } P = 3 E_{ph} \cdot I_{ph} \cdot \cos \phi = \sqrt{3} V_L \cdot I_L \cdot \cos \phi = W$$

$$Q = 3 E_{ph} \cdot I_{ph} \cdot \sin \phi = \sqrt{3} V_L \cdot I_L \cdot \sin \phi = V_A \cdot R$$

$$S = 3 E_{ph} \cdot I_{ph} = \sqrt{3} V_L \cdot I_L = V_A$$

Star connection: ($V_L = \sqrt{3} E_{ph}$, $I_L = I_{ph}$, V_L leads by 30°)

Delta connection: ($V_L = E_{ph}$, $I_L = \sqrt{3} I_{ph}$, I_L lags by 30°)

→ α -Wattmethod:

Two coils namely:- Potential/Voltage coil & Current coil.

~~Notes~~ High Fesib, low X Low Fesib, high X


$$W_1 + W_2 = \sqrt{3} V_L \cdot I_L \cdot \cos \phi = P$$

$$\sqrt{3}(W_1 - W_2) = \sqrt{3} V_L \cdot I_L \cdot \sin \phi = Q$$


$$\phi = \tan^{-1} \left[\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right]$$

3.2. Problems on Power Measurement

2-Wattmeter Method

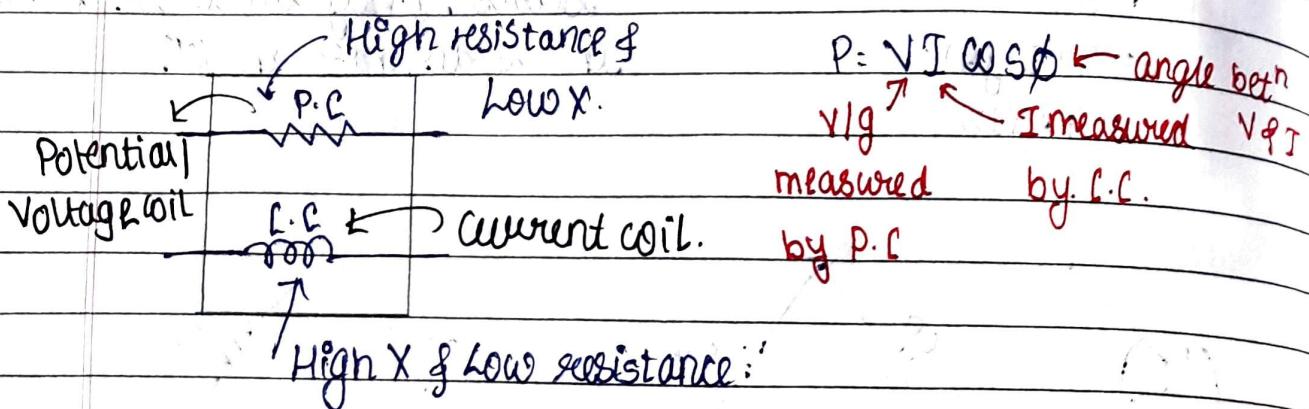

* DERIVATION:

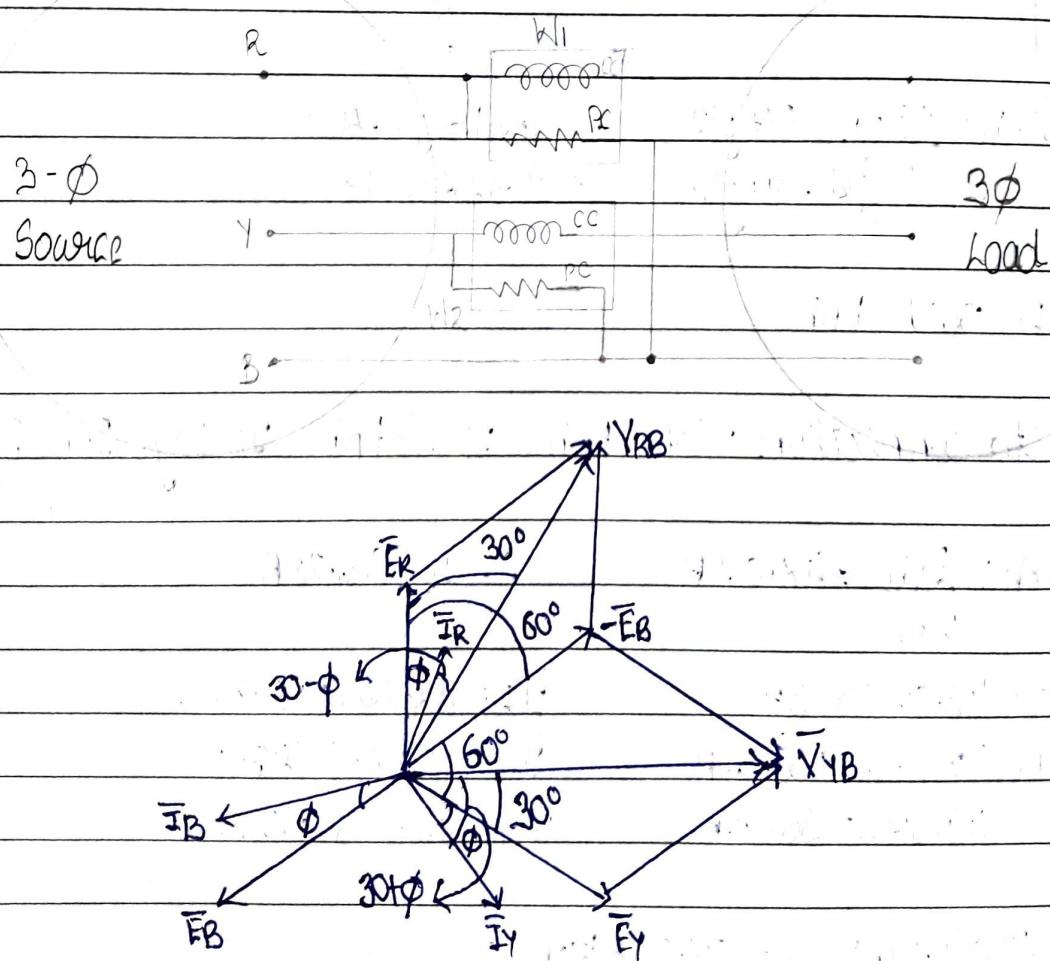

$$W_1 = V_{RB} I \cdot \cos(30 - \phi) = V_L I_L \cdot \cos(30 - \phi)$$

$$W_2 = V_{RB} I \cdot \cos(30 + \phi) = V_L I_L \cdot \cos(30 + \phi)$$

$$W_1 + W_2 = V_L I_L \cdot [\cos(30 + \phi) + \cos(30 - \phi)]$$

$$= V_L I_L \cdot 2 \cos 30^\circ \cdot \cos \phi$$

$$W_1 + W_2 = V_L I_L \cdot \left[2 \times \frac{\sqrt{3}}{2} \times \cos \phi \right]$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi = P$$

$$W_1 - W_2 = V_L I_L \cdot [\cos(30 - \phi) - \cos(30 + \phi)]$$

$$= V_L I_L \cdot [2 \sin 30^\circ \cdot \sin \phi]$$

$$= V_L I_L \sin \phi$$

$$Q = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} (W_1 - W_2)$$

$$\tan \phi = \frac{Q}{P} = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}$$

$$\therefore \phi = \tan^{-1} \left[\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right]$$

SR.NO.	PARAMETERS	$\phi = 0$	$\phi = 60^\circ$	$\phi = 90^\circ$	$\phi = -60^\circ$	$\phi = -90^\circ$
1.	$\cos \phi$	1	0.5 (lag)	0 (lag)	0.5 (lead)	0 (lead)
2.	Load	Resistive	Inductive	Purely Induc	Capacitive	Purely Cap
3.	W_1	+ve	+ve	+ve	0	-ve
4.	W_2	+ve	0	-ve	+ve	+ve
5.	MESC	$P = 2W_1 - 2W_2$ $P = W_1, W_2 = 0$ $\therefore W_1 = W_2$	$P = 0$	$ W_1 = W_2 $	$P = W_2$ $\therefore W_1 = 0$	$P = 0$ $ W_1 = W_2 $

→ AC CIRCUITS:

1. Series Resonance.

$$X_L = X_C$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

~~$$I_0 X_L = I_0 X_C$$~~

$$V_{L0} = V_{C0}$$

→ Cut-off frequencies

→ Bandwidth

$$\omega_1 = \omega_0 - \frac{R}{2L} \text{ rad/s} \quad \omega_2 = \omega_0 + \frac{R}{2L} \text{ rad/s}; \Delta\omega = \frac{R}{L} \text{ rad/s}, \Delta f = \frac{R}{2\pi L} \text{ Hz}$$

$$f_1 = f_0 - \frac{R}{4\pi L} \text{ Hz}, \quad f_2 = f_0 + \frac{R}{4\pi L} \text{ Hz}$$

$$\rightarrow Q.F.: - \frac{V_{C0}}{V} = \frac{V_{L0}}{V} = \frac{1}{R\sqrt{C}} = \frac{\omega_0}{\Delta\omega}$$

2. Parallel Resonance:

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}, f_0 = \frac{1}{2\pi\sqrt{LC}} \frac{1 - R^2}{L^2} \text{ Hz}$$

~~$$Q.F.: I_0 = \frac{V}{LRC} = \frac{V}{Z_0} \Rightarrow Z_0 = L \frac{1 - R^2}{R^2} \text{ ohms}$$~~

$$Q.F.: \frac{X_{L0}}{R} = \frac{\omega_0 L}{R}$$