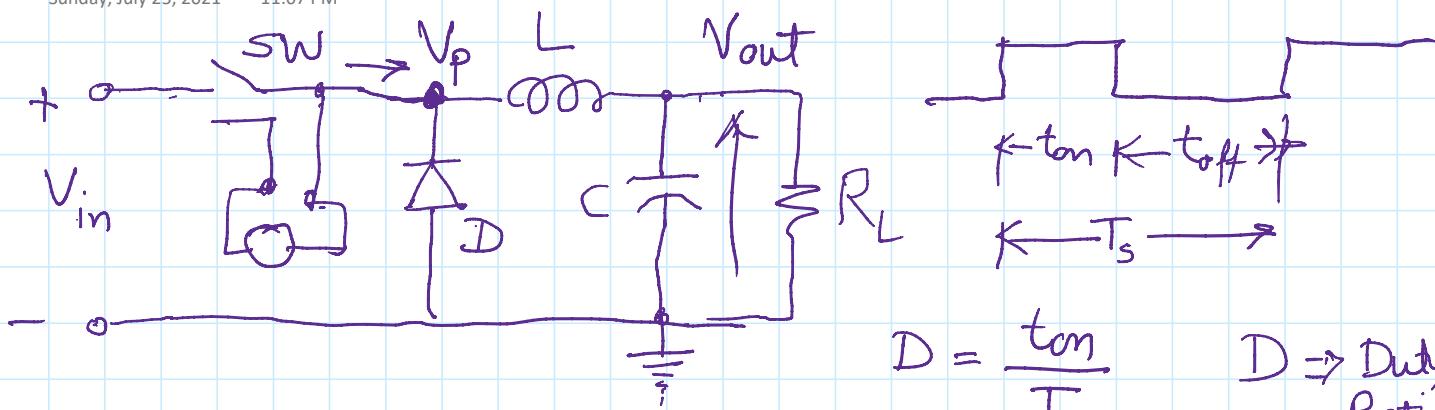


## Buck Converter

Sunday, July 25, 2021 11:07 PM

Assume Cont. Conduction mode ; Sw + Diode are ideal



When the switch is on \$t = t\_{on} \Rightarrow t\_{on} = DT\_s

$$\text{Diode is OFF } V_p = \int_0^{t_{on}} V_{in} \cdot dt = V_{in} \times D T_s ; V_{out} = V_c(t)$$

When the switch is OFF

$$\text{Diode is ON } V_p = \int_{T_{off}} V_{in} dt = V_{in} (1-D) T_s = 0 \\ V_{out} = V_c(t)$$

If \$V\_L \text{ avg} = 0\$ Over One Switching Cycle \$\Rightarrow V\_{p(\text{avg})} = V\_{out}  
 $\therefore D = V_{out}/V_{in}$

Assumption \$\rightarrow\$ (i) The SW and D are ideal

- Property of L and C
  - (ii) The average inductor voltage during a complete cycle is zero
  - (iii) The average cap. voltage during one complete switching cycle is zero
  - (iv) The load current is constant with switching ripples - \$(I\_0)\$
- We can

Let inductor current ripple is K % of \$I\_0\$

Let inductor current ripple is  $K\%$  of  $I_o$

The capacitor voltage ripple is  $\varrho\%$  of  $V_{out}$

Typically  $K$  is  $10\%$  to  $20\%$  →  $K_{max} = 20\%$  of  $I_o$

Typically  $\varrho$  is  $2\%$  to  $5\%$  of  $V_{out}$  →  $\varrho_{max} = 5\%$

a) To find  $L$  value let  $K = 0.1$  ( $10\%$ )

The volt-second product is zero over a complete cycle


$$U_L = L \frac{di}{dt} = L \frac{\Delta I}{\Delta t}$$

If we consider on time

$K$  is per unit

$$U_L = (V_{in} - V_{out}) = L \frac{K I_o}{T_{on}} = L \frac{K I_o}{D T_s}$$

$$\left. \right\} T_s = \frac{1}{f_s}$$

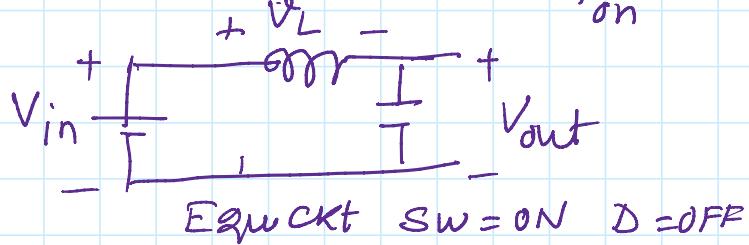

$$L = \frac{D (V_{in} - V_{out})}{K I_o \cdot f_s}$$

$D$  &  $K$  are in p.u.


$$L_{min} = \frac{D_{min} (V_{in(max)} - V_{out})}{(K I_o) \times f_s}$$

$$D_{min} = \frac{V_{out}}{V_{in(max)}}$$

$\Delta I_L$

⑥ To find  $C_{min} \Rightarrow$

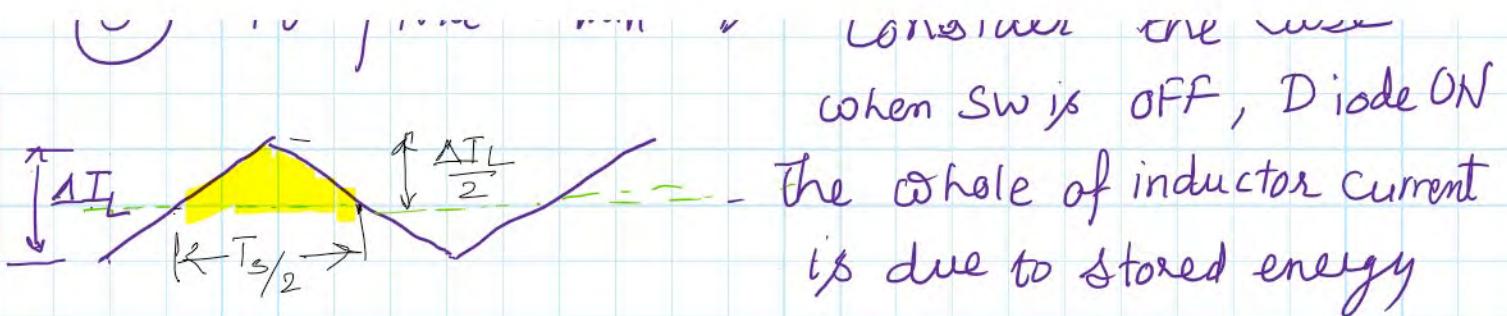Consider the case when  $S_w$  is OFF, Diode ON



$$\therefore i_c = C \frac{dV_c}{dt} = C \frac{\Delta V_0}{dt} \Rightarrow$$

$$i_c dt = C_{\min} \Delta V_0 = \text{Area under the curve}$$

$$\frac{L}{2} \times \frac{\Delta I_L}{2} \times \frac{T_s}{2} = C_{\min} \Delta V_0$$

$$\therefore \boxed{C_{\min} = \frac{\Delta I_L}{8 f_s \Delta V_0}}$$

$$\Delta I_L = R I_o$$

$$\Delta V_o = \mathcal{R} V_{out}$$

$\mathcal{R}$  and  $\mathcal{R}$  are in p.u.

### (c) Average Switch Current

$$D = \frac{V_{out}}{V_{in}} = \frac{I_{in}}{I_{out}}$$

$$I_{sw(\text{ave})} = I_{in(\text{ave})}$$

$$V_{out} \times I_{out} = P_{out} = V_{in(\min)} \times I_{in(\text{ave})}$$

$$\therefore I_{in(\text{ave})} = \frac{P_{out}}{V_{in(\min)}}$$

### (d) The average Diode Current

The Diode Carries Current only during OFF time

$$I_{diode(\text{ave})} = T_{off} (1-D) \cdot I$$


$$\therefore -I_{\text{diode(Are)}} = I_{\text{out}} \left( \frac{U}{V} - \frac{U}{V_{\text{min}}} \right)$$


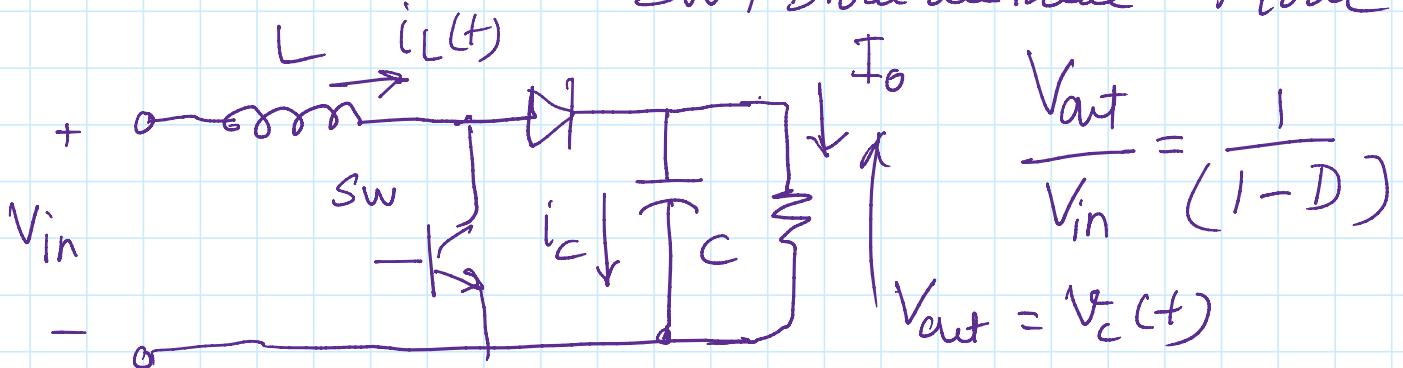
## Boost Converter

Monday, July 26, 2021 12:30 AM

Assume Continuous Conduction  
SW + Diode are ideal Mode



\* When the Switch is ON, the inductor stores energy  $\rightarrow V_{sw} = 0$  ideally  $V_L(t) = V_{in}$

the inductor current does not transfer its energy to the output load since the diode is OFF

the capacitor Supplies its stored energy to the load (Discharges)

\* When the Switch is OFF  $(1-D) T_s = t_{off}$

the inductor transfers its stored energy to the load, the Diode is ON

and also charges the capacitor from Supply input

a) To find  $L$

$$V_L(\text{ave}) = 0 \quad V_L \text{ during ON state}$$

$$V_L = V_{in}$$

$$V_L = L \frac{di}{dt} = L \frac{\Delta I_L}{D \cdot T_s} = V_{in}$$

$$\therefore L = \frac{D V_{in}}{\Delta I_L \cdot f_s} \quad \overline{D \cdot T_S} = v_{in}$$

$\Delta I_L$  can be expressed  
as  $k I_{out}$ ;  $D \Rightarrow$  Per unit  
 $f_s$  is in Hz      Duty

⑥ To find C value  $\rightarrow$

During SW ON state  $\rightarrow (D T_S)$

Capacitor current is

$$i_C(t) = C \frac{dV_C}{dt} = \frac{C \Delta V_0}{D \cdot T_S} = I_{out}$$

$$\therefore C = \frac{D I_{out}}{f_s \Delta V_0}$$

$$\Delta V_0 = \mathcal{R} \times V_{out}$$

$\mathcal{R}$  is per unit o/p voltage  
ripple

⑦ Average Switch Current =  $D \cdot I_{input}$

$$V_{in} \times I_{in} = V_{out} I_{out} = P_{out}$$

$$I_{SW(Ave)} = D \times \frac{P_{out}}{V_{in}}$$

d-

The average Diode Current is

$$I_{\text{Diode(Ave)}} = (1 - D) I_{\text{in}} = (1 - D) \frac{P_{\text{out}}}{V_{\text{in}}}$$




## Buck-Boost Converter

Monday, July 26, 2021 1:01 AM

Assume Continuous Current

Conduction mode and

$S_W$  + Diode are ideal

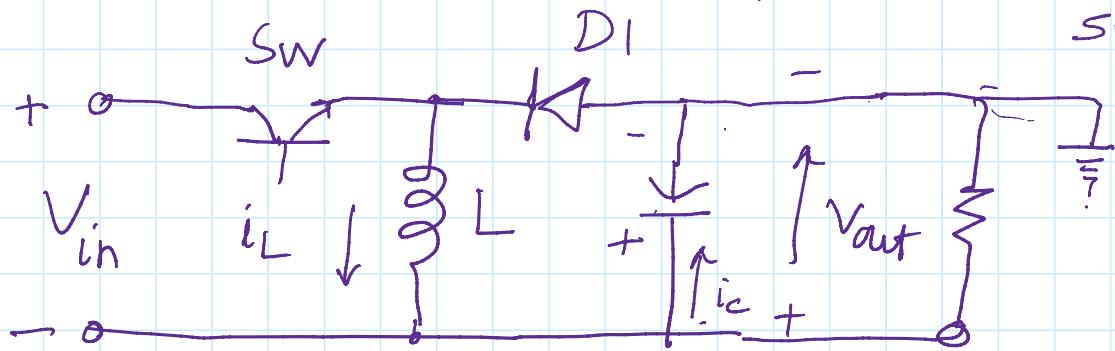

The voltage transfer Ratio is

$$\frac{V_{out}}{V_{in}} = -\frac{D}{1-D}$$

For  $D > 0.5 \rightarrow V_{out} > V_{in}$  Boost Mode

For  $D < 0.5 \rightarrow V_{out} < V_{in}$  Buck Mode

For  $D = 0.5 \rightarrow V_{out} = V_{in}$

- During  $S_W$  ON state

inductor stores energy since  $D_I$  is OFF

Only Cap stored energy is transferred to the load with appropriate polarity

- During  $S_W$  OFF state, Diode  $D_I$  Starts Conducting

- The inductor supplies / transfer the stored energy to the load, the inductor current completes its negative half cycle.

energy to the load, the inductor current completes its path through diode, which is ON during this period

The capacitor also gets charged during this process -

If  $D > 0.5 \rightarrow$  the inductor stores more energy and hence boost action is possible

If  $D < 0.5 \rightarrow$  The inductor stores less energy and hence buck action is possible -

(a) To find  $L$

Consider the period when SW is ON

$$V_L(t) = V_{in} = L \frac{di}{dt} = L \frac{\Delta I_L}{D \cdot T_s}$$

$$\therefore L = \frac{V_{in} \cdot D}{\Delta I_L \cdot f_s}$$

$$\Delta I_L = K I_0$$

$K$  is per unit ripple

$V_{in}$  may vary from  $V_{in(\min)}$  to  $V_{in(\max)}$

- which gives us  $D_{\max}$  &  $D_{\min}$

$$D_{\min} = \frac{V_{out}}{V_{in(\max)} + V_{out}}$$

}  $V_{out}$  is constant in all operations

$$D_{max} = \frac{V_{out}}{V_{in(max)} + V_{out}}$$

in all operations

$$L_{min} = \frac{V_{in(max)} D_{min}}{\Delta I_L \cdot f_s}$$

$$\Delta I_L = K I_0$$

⑥ To find C

The capacitors will discharge its energy during  $S_w = ON$  and diode is OFF

$$i_c(t) = I_{out} = C \frac{dV_C}{dt} = \frac{C \Delta V_0}{D \cdot T_S}$$

$$C = \frac{D I_{out}}{\Delta V_0 \cdot f_s}$$

$$C_{min} = \frac{D_{min} \times I_{out}}{\Delta V_0 \cdot f_s}$$

$$\Delta V_0 = \underline{r} V_{out}$$

$\underline{r}$  = Per unit op voltage ripple

ripple

(c) What is the average switch current?

$$I_{SW(\text{ave})} = I_{in(\text{ave})}$$

$$P_{out} = V_{out} \cdot I_{out} = V_{in} \cdot I_{in(\text{ave})}$$

The average switch current would also vary for  $I_{min}$  and  $I_{max}$

$$\therefore I_{SW(\text{ave})} = \frac{P_{out}}{V_{in(\text{min})}} \rightarrow \text{Worst Case Scenario} -$$

(d) What is the average diode current?

$$I_{diode(\text{ave})} = I_c(\text{ave}) + I_{out}$$

$$I_c(\text{ave}) = 0 \text{ over a complete cycle}$$

$$\therefore I_{diode(\text{ave})} = I_{out} = \frac{P_{out}}{V_{out}}$$

