

# Converters: Buck, Boost, Buck-Boost

M	T	W	T	F	S	S
Page No.:						YOUVA
Date:						


Convertors :-

- ① AC - AC converter  $\rightarrow$  transformer
- ② AC - DC  $\rightarrow$  rectifier
- ③ DC - AC  $\rightarrow$  Inverter
- ④ DC - DC  $\rightarrow$  chopper 3

We will learn this

for DC - DC conversion we want this as we want these voltages of different levels for different applications from same source. So we need these

for this we use

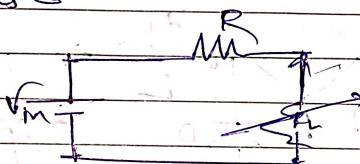

We want  $R_L$  should have  $V_o$  output so.

$$V_{in} - IR - IR_L = 0 \quad I = \frac{V_{in}}{R+R_L}$$

$$IR_L = V_o \quad \text{So, } I = \frac{V_o}{R_L}$$

$$\frac{V_o}{R_L} = \frac{V_{in}}{R+R_L}$$


$$\frac{1+R}{R_L} = \frac{V_{in}}{V_o}$$

$$\left(1 - \frac{V_{in}}{V_o}\right) = \frac{R}{R_L}$$

$$\left[ R_L = \frac{R \cdot V_o}{V_o - V_{in}} \right]$$

$$\left[ R_L = R \left(1 - \frac{V_{in}}{V_o}\right)^{-1} \right]$$

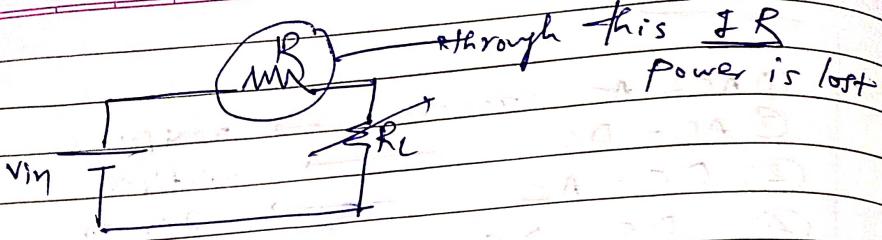
so, we can have this resistor in series & get desired output. But here



But here If we increase current instead of trying to reduce voltage we can achieve same behaviour as load is constant.


$$\text{So } \underline{v = IR} \quad \underline{\& JT = V_L}$$

let's do it.

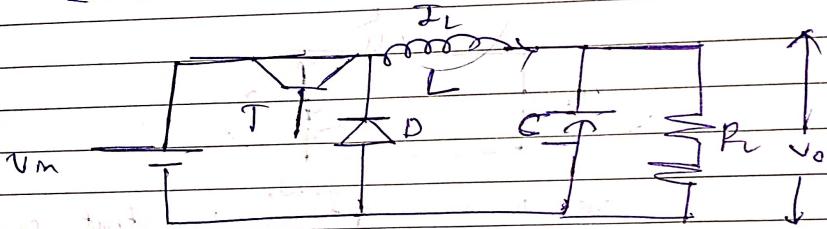


Now we want that the current through  $C$  & all ripple through  $C$  Why? Because of DP ST.

So Now for  $T_{on}$

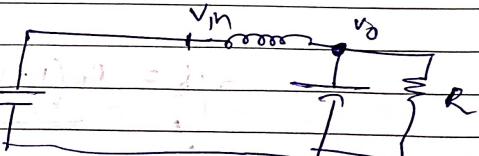
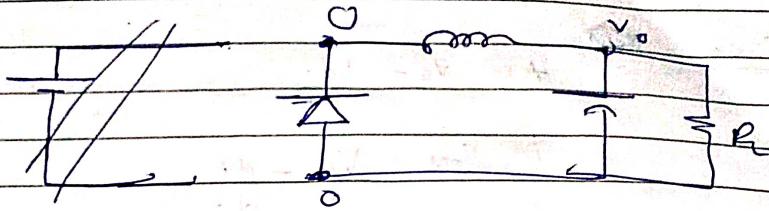
$$\underline{V_L = V_{in} - V_o} \quad \text{for } T_{on}$$




$$\text{So, } V_L = -V_0$$

Now

As we want that All Ripple should go through a  
filter means avg  $\bar{I}_C = 0$ .
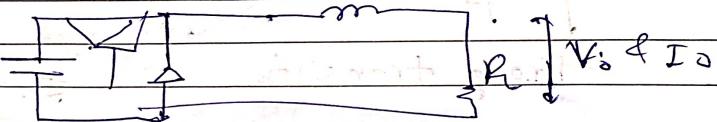
$$\text{So, } \bar{I}_B = \bar{I}_C \rightarrow \text{As Direct series}$$



Now fly we want  $\underline{V_L \text{ avg}} = 0$  so that  $\underline{V_0 = \Delta V_C}$

$$\underline{\underline{V_L \text{ avg}}} = 0$$

$$(V_{in} - V_0) \frac{d}{T_S} + (C - V_0) \frac{d}{d} T_S = 0$$

$$V_{ind} - V_{0d} - V_0 + V_{0f} = 0$$

$$\boxed{V_0 = V_{ind}}$$

By V<sub>sec</sub> balance

$$\begin{aligned} \cancel{T_{on}} &= d \\ \cancel{T_{on}} + \cancel{T_{off}} & \\ T_S &= T_{on} + T_{off} \end{aligned}$$

$$T_{on} = d \quad \boxed{T_S = T_{on} + T_{off}}$$

$$\cancel{T_{on}} = (1-d) T_S$$

$$\cancel{T_{off}} = (d-1) T_S$$


Now

$$\Delta I \quad V_L = \frac{L di}{dt}$$

$$\text{for } T_{ON} \quad V_L = \frac{di}{dt}$$

$$V_o - V_m = \frac{di}{dt}$$
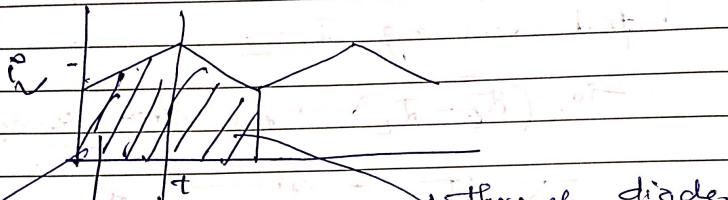
$$= \frac{V_o - V_m}{L} = \frac{di}{dt}$$



$J_{DS}$


through transistor

through diodes

$J_D (t)$

$J_D (t) \text{ avg}$

$$\text{But } [\text{Avg} = \rho_a]$$

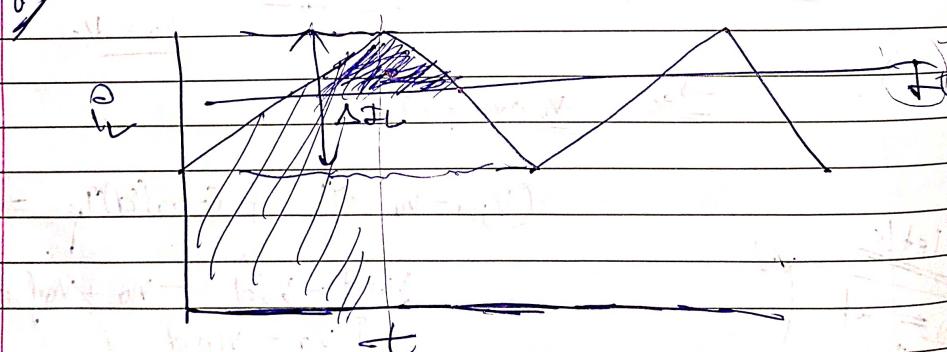

$\underline{\underline{I_o}}, \text{ now}$

$$I_o \quad \Delta Q = \frac{1}{2} \times \frac{\Delta I_L}{2} \times \frac{T_s}{2}$$

there goes

$$\Delta Q = \frac{\Delta I_L T_s}{8}$$

$$\Delta Q = C \Delta V$$

$$C \Delta V = \frac{\Delta Q_L}{8f_S}$$

extra

$$\Delta Q_C = \frac{d(C-d)}{8f_S L C}$$

$C = \frac{\Delta Q_L}{8f_S (\Delta V_C)}$

$\Delta V_C$

Now,

$$\frac{V_L}{L} = -\frac{di}{dt}$$

$$\text{For Topff } V_0 = -\frac{V_L}{L}$$

$$\frac{V_0}{L} = \frac{di}{dt}$$

$$\frac{dV_0}{dt} = \frac{di}{dt}$$

~~$$\frac{V_0}{L} = \frac{\Delta V_{in}}{\Delta Q_L}$$~~

$$\frac{V_0}{L} = \frac{di}{dt}$$

$$(1-d) T_S V_0 = \frac{\Delta Q_L}{L}$$

$L = \frac{(1-d)V_0 T_S}{\Delta Q_L}$

Always considered  $L$  to be minimum if two come

# Buck

Conclusion :-

$$\sigma = v/m d$$


$$f_p = I_{Lavg}$$

$$L = \frac{(1-d)v_0 T_s}{\Delta I_L}$$

$$T_s = \frac{1}{f_s}$$

Always to  
be minimum

$$L = \frac{(1-d)v_0}{f_s \Delta I_L}$$

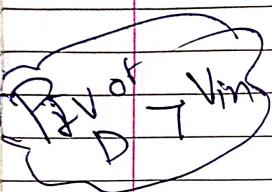

$$C = \frac{\Delta I_L}{8 f_s \Delta V_C}$$

$$I_{Lavg} = I_o \quad \Delta V_{Lavg} = 0$$


$$\Delta I_{Cavg} = 0 \quad \Delta V_{Cavg} = V_o$$

$$I_{drain avg} = f_L(1-d) = I_o(1-d)$$

$$I_{trash avg} = f_L d = I_o d$$

$$V_o = V_{ind}$$

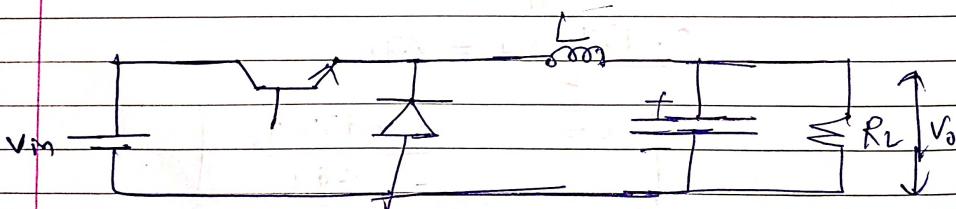
$$\text{At } T_{on} \quad V_L = V_{in} - V_o \quad \text{At } T_{off} \quad V_L = -V_o$$




for  $I_{on}$



$T_{off}$

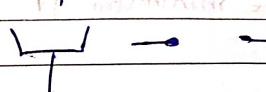

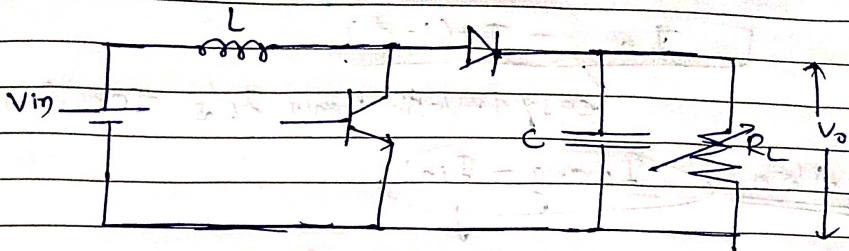Boost converter:-

② V sec balance (across L) (To find relation  $V_{in}$  &  $V_o$ )

$$\text{for } T_{ON} \quad V_L = V_{in}$$

$$\text{for } T_{off} \quad V_L = V_{in} - V_o$$

$$V_{in}dT_S + (V_{in} - V_o)(C(1-d))T_S = 0$$

$$V_{in}d + V_{in} - V_o - V_{in}d + V_o(1-d) = 0$$

$$V_{in} - V_o(1-d) = 0$$

$$\boxed{V_{in \ avg} = 0}$$


$$V_{in} = V_o(1-d)$$

$$\boxed{V_o = \frac{V_{in}}{1-d}}$$

③ Current - see balance (across C) (To find  $I_{L \ avg}$ )

$$\begin{cases} IV_C = V_o \\ I_{C \ avg} = 0 \end{cases}$$

for  $T_{ON}$

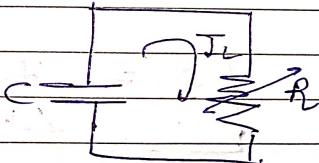

$$\boxed{I_C = -I_o}$$

$$\text{for } T_{off} \quad I_C = I_L - I_o$$

$$-I_o d T_S + (I_L - I_o)(1-d)T_S = 0$$

$$-I_o d + I_L - I_o - I_o d + I_o d = 0$$

$$\boxed{I_L(1-d) = I_o}$$

$$I_o = I_i(1-d)$$

easy trick that only  $I_o$ 's second will be  $I_o$

Also


$$I_{avg} = I_m$$

as Always same

## ⑧ Current across Capacitor (for C)

$$T_{on} \quad I_c = -I_o$$

$$T_{off} \quad I_c = I_{oi} - I_o$$

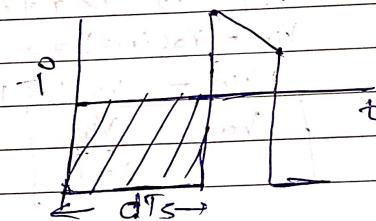

$$\Delta Q = I_o dTs$$

$$C \Delta V_c = I_o dTs$$

$$C = \frac{I_o dTs}{\Delta V_c}$$

$$C = \frac{I_o d}{\Delta V_c f_s}$$

~~Current / Voltage~~  
 Voltage across Inductor C for L)


$$T_{ON} \rightarrow V_L = L \frac{dI}{dt}$$

$$\frac{V_L}{L} = \frac{dI}{dt} \quad V_L = V_{in}$$

$$\frac{di}{dt} = V_m$$

$$T_{OFF} : V_L = V_{in} - V_o$$

$$\frac{V_m - V_o}{L} = \frac{di}{dt}$$

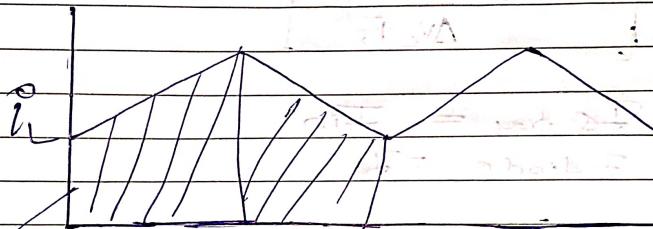

~~avg~~  
~~V\_m~~  
~~dI/dt~~

$$V_{in} = \frac{dI}{dt}$$

$$\frac{dI}{dt} = \frac{V_m}{L}$$

$$L = \frac{dI}{dV_m}$$

$$L = \frac{V_m \Delta I}{f_s}$$

$\rightarrow L$  to be minimum

for  $I_0 = I_{in}$   
transistor

$$I_D = I_0$$

Summary

$$\boxed{V_o = \frac{V_{in}}{1-d}}$$

$$\boxed{I_o = I_L(1-d)}$$

$$\boxed{I_{L\text{avg}} = 2I_n}$$

$$\boxed{V_{L\text{avg}} = 0}$$

$$\boxed{V_{C\text{avg}} = V_o}$$

$$\boxed{V_{C\text{avg}} = 0}$$

$$\boxed{L = \frac{V_{in}d}{\Delta f_L f_s}}$$

$L$  to minimum


$$\boxed{C = \frac{I_o d}{\Delta V_C f_s}}$$

$$\text{avg } I_{D\text{ tray}} = I_{in}$$


$$\text{avg } I_{\text{diode}} = I_o$$

$$T_{on} \rightarrow V_L = V_m \quad T_{off} \rightarrow V_L = V_{in} - V_o$$
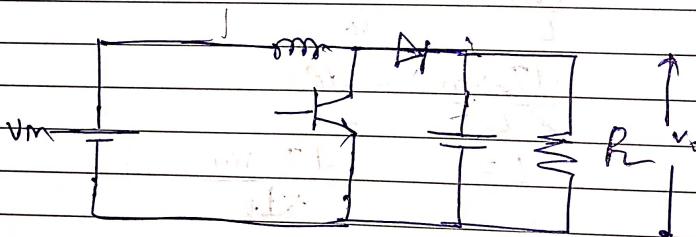
$$V_c = -I_o \quad \rightarrow I_C = I_L - I_o$$



*ppv of D  $V_o$*

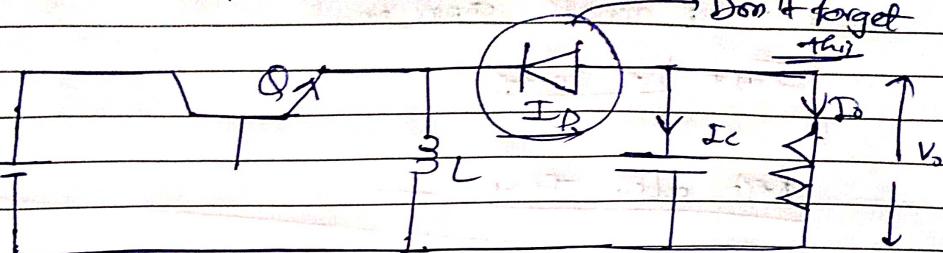Buck - BoostVolt second :-

$$T_{ON} \quad V_L = V_{in}$$

$$T_{off} \quad V_L = V_o$$

$$V_{ind} + V_{o(1-d)} = 0$$

$$V_{ind} + V_o - V_{od} = 0$$

$$\boxed{V_o = -\frac{V_{ind}}{1-d}}$$

(→ for sign ✓)

Current second :-

$$T_{ON} \quad I_c = -I_o$$

$$T_{off} \quad I_c = I_L - I_o$$

$$-I_{od} + (I_L - I_o)(1-d) = 0$$

$$-I_{od} + I_L - I_o - I_{od}(1-d) + I_{od}(1-d) = 0$$

$$I_L(1-d) = I_o$$

$$\boxed{I_L = \frac{I_o}{1-d}}$$

$$\boxed{I_o = I_L(1-d)}$$

only  $I_{off}$  or  $I_L$  going

current across Capacitor :-

Just the same

Rest also same :-

Summary

$$V_o = \frac{-V_m d}{1-d}$$

$$I_o = I_c (1-d)$$

$$I_L \text{ avg} = I_m$$

$$M \text{ avg} = 0$$

$$V_c \text{ avg} = V_0$$

$$I_c \text{ avg} = 0$$

L  $\rightarrow$   $I_L = \frac{V_m d}{\Delta V_{c,f}}$

$$C = \frac{I_o d}{\Delta V_{c,f}}$$




$$\text{avg } I_p = I_m \quad \text{avg } I_d = I_o$$

$$\text{For } V_L = V_m$$

$$\rightarrow I_c = -I_o$$

$$\text{For } V_i = V_0$$

$$I_E = I_L - I_o$$

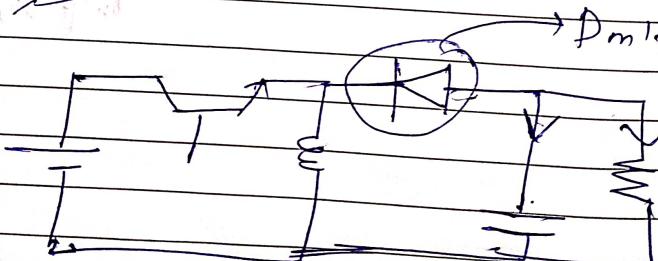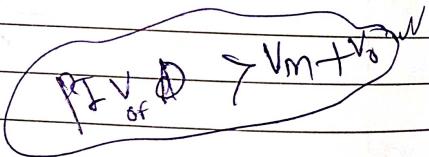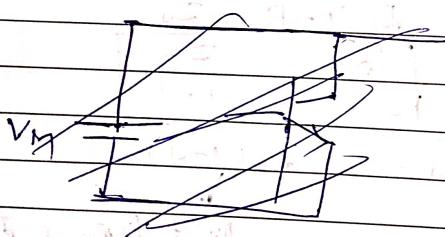

Suppose  $0.1 \text{ A}$  or  $50 \text{ mA}$  to  $20 \text{ mA}$

1-d Page  $\rightarrow$  Page of  $d$  in J.M.

$\Delta I =$  ~~variable around~~  
to output

$$P = VI$$

$$V_{out} = V_{in} + \Delta V$$

Ans for  $\Delta V$

consider  $|d|$  according  $(V_{pn})$  & Not  $V_{min} < d_{min}$  is  
 $\frac{\Delta V}{V_{out}}$  is same

4 steps

to derive

Voltage second balance for ~~for~~  
current second balance for ~~for~~

$\frac{di}{dt}$  Current across capacitor  
Voltage across inductor

$$\frac{dV_L}{dt} = \frac{di}{dt} V_L$$

$I_{Lavg}$   $V_{Lavg}$   
 $I_{Cavg}$   $V_{Cavg}$   
 $L$ ,  $C$   $I_{Lavg}$   $I_{Cavg}$

steps of question

find always 1 first for ~~so that~~ minimum  
 $L$  you get d

don't forget  $V_m$  accordingly

J.M

$P_{out} = P_{in}$   $\Rightarrow \eta = 100\%$