

Introduction of Active and Passive Components and Verification of Kirchhoff's Laws using circuit simulation

Name: Adwait S Purao
UID: 2021300101
Branch: Computer Engineering
Batch: B2

OBSERVATION TABLE:**1) Resistance**

Sr. No.	Value of R using colour code	Value of R using multimeter	%Error
1	$22 * 10^2 \pm 5\%$	$22.2 * 10^2$	-0.9%
2	$10 * 10^2 \pm 5\%$	$9.98 * 10^2$	0.2%



2) Inductor

Sr. No.	Value of L using colour code	Type of Inductor
1	$10 * 10^3$	Axial
2	$56 * 10^2$	Axial

3) Capacitor

Sr. No.	Value of C	Type of Capacitor
1	$100 * 10^{-6}$	Electrolytic
2	$1000 * 10^{-6}$	Electrolytic
3	$104 * 10^{-9}$	Paper
4	$224 * 10^{-9}$	Paper

4) Active Components

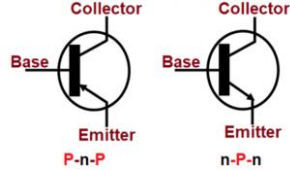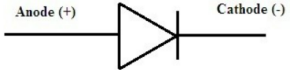Sr. No.	Name of the component	Symbol	Identification of pins form observation	No. printed on component to refer datasheet
1	Transistor		Emitter, Base, Collector	BC547 K944
2	Diode		Anode, Cathode	IN4007

EXPERIMENT No: 1

DATE: 20 / 6 / 2022

Introduction of Active and Passive Components & Verification of Kirchoff's Laws using circuit simulation

AIM:

- 1) To differentiate active and passive components from the given components.
- 2) To identify the value of resistors using colour codes and wattage according to size of the resistors. Also verify the value using multimeter.
- 3) To find different types of capacitors and their values.
- 4) To identify the pins of transistor and diodes.
- 5) To verify Kirchhoff's Laws using circuit simulation with the help of SEQUEL.

APPARATURUS & COMPONENTS REQUIRED:

Different active and passive components, Digital Multimeter, Sequel simulator

THEORY: Write theory related with following questions.

- 1) Define active and passive components. Give examples of each.
- 2) Write statement of Kirchhoff's laws.

Procedure:

- 1) Find the value of given resistors using color code also verify it using given multimeter.
- 2) Find the value of the given inductor.
- 3) Find the value of given capacitor also identify types of capacitors.
- 4) Identify the terminals in case of Diode and Transistor. Also write down the number given on transistor and diode and refer its datasheet.
- 5) Download SEQUEL Simulator.
- 6) For verification of Kirchhoff's Laws, built the circuit in simulator.
- 7) Simulate the circuit and obtain current flowing through each resistor and voltage across each resistor.
- 8) Verify the result using Kirchhoff's current equation for the respective node.
- 9) Verify the result using Kirchhoff's voltage equation for the present 3 loops in the circuit.
- 10) Verify them with theoretical values.

Active components: An active component is an electronic component which supplies energy to a circuit.


Eg. Voltage sources, Current sources. Generators (such as alternators and DC generators), All different types of transistors (such as bipolar junction transistors, MOSFETS, FETs, and JFET).,Diodes (such as Zener diodes, photodiodes, Schottky diodes, and LEDs)

Passive components: A passive component is an electronic component which can only receive energy, which it can either dissipate, absorb or store it in an electric field or a magnetic field. Passive elements do not need any form of electrical power to operate.

Eg. Resistors, Inductors, Capacitors, Transformers

Kirchhoff's laws:

- **Kirchhoff's current law:** Kirchhoff's Current Law states that the total current entering a junction or a node equals the charge leaving the node as no charge is lost.
- **Kirchhoff's voltage law:** Kirchhoff's voltage law states that the voltage around a loop equals the sum of every voltage drop in the same loop for any closed network and equals zero.

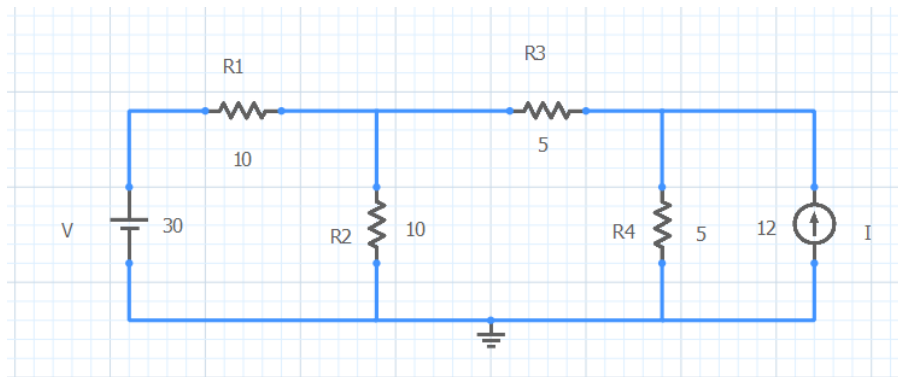CIRCUIT DIAGRAM:**Sequel Implementation**

	Variable	Value
1	I1	3.552714e-016
2	V1	3.552714e-015
3	I2	3.000000e+000
4	V2	3.000000e+001
5	I3	-3.000000e+000
6	V3	-1.500000e+001
7	I4	9.000000e+000
8	V4	4.500000e+001

Sequel Output**OBSERVATION TABLE:**

V ₁ (Volts)	V ₂ (Volts)	V ₃ (Volts)	V ₄ (Volts)
0	30	-15	45

I ₁ (A)	I ₂ (A)	I ₃ (A)	I ₄ (A)
0	3	-3	9

CALCULATIONS:

classmate
Date _____
Page _____

$i_3 = -12 \text{ A}$

Applying KVL to Mesh I.

$$30 - 20i_1 + 10i_2 = 0$$

$$-2i_1 + i_2 = -3 \quad \text{--- (1)}$$

Applying KVL to Mesh II.

$$-20i_2 + 10i_1 + 5i_3 = 0$$

$$-20i_2 + 10i_1 + 5(-12) = 0$$

$$-20i_2 + 10i_1 - 60 = 0$$

$$i_1 - 2i_2 = 6 \quad \text{--- (2)}$$

Solving eqⁿs (1) & (2),

$$i_1 = 0 \text{ A}$$

$$i_2 = -3 \text{ A}$$

& $i_3 = -12 \text{ A}$

$\therefore i_{R1} = i_1 = 0 \text{ A}$

$$i_{R2} = i_1 - i_2 = 3 \text{ A}$$

$$i_{R3} = -3 \text{ A}$$

$$i_{R4} = i_2 - i_3 = -3 + 12 = 9 \text{ A}$$

$$V_{R_1} = i_{R_1} \cdot R_1 = 0$$

$$V_{R_2} = i_{R_2} \cdot R_2 = 30V$$

$$V_{R_3} = i_{R_3} \cdot R_3 = -15V$$

$$V_{R_4} = i_{R_4} \cdot R_4 = 45V$$

RESULT:

V ₁ (Volts)		V ₂ (Volts)		V ₃ (Volts)		V ₄ (Volts)	
Theoretical	By simulation	Theoretical	By simulation	Theoretical	By simulation	Theoretical	By simulation
0	0	30	30	-15	-15	45	45

I ₁ (A)		I ₂ (A)		I ₃ (A)		I ₄ (A)	
Theoretical	By simulation	Theoretical	By simulation	Theoretical	By simulation	Theoretical	By simulation
0	0	3	3	-3	-3	9	9

CONCLUSION:

We studied different types of capacitors, resistors and inductors and their applications, we also deciphered their values using color coding. We learnt about Kirchhoff's Laws and implement a circuit and found out current through each branch and verified using sequel software