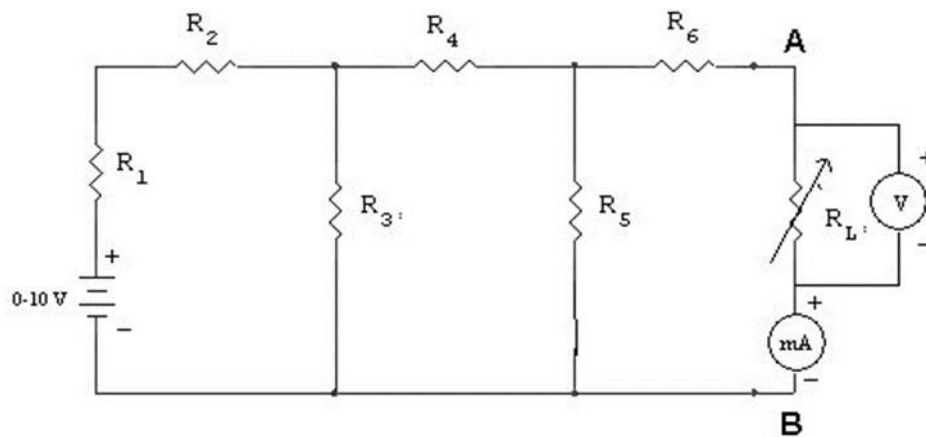


Name: ADWAIT S PURAO

UID: 2021300101

Branch: Comps B (Batch B2)

**Verification of Thevenin's, Norton's and
Maximum Power Transfer Theorem**

CIRCUIT DIAGRAM:**OBSERVATIONS:**

$R_1 = 0\ \Omega$, $R_2 = 100\ \Omega$, $R_3 = 330\ \Omega$, $R_4 = 100\ \Omega$, $R_5 = 330\ \Omega$, $R_6 = 470\ \Omega$, $V_1 = 10\ \text{V}$

Sr. No.	$R_L\ (\Omega)$	$V_L\ (\text{V})$	$I_L\ (\text{mA})$	$P_L\ (\text{mW})$
1	383	2.046	5	10.23
2	403	2.088	5	10.44
3	423	2.146	4.95	10.62
4	443	2.202	5	11.01
5	463	2.246	5	11.23
6	483	2.275	5	11.375
7	503	2.360	4.75	11.21
8	523	2.405	4.6	11.063
9	543	2.451	4.5	11.029
10	563	2.497	4.4	10.987

$V_{Th}\ (\text{V})$	$R_{Th} = R_N\ (\Omega)$	$I_N\ (\text{mA})$
5.01	582	8

CALCULATIONS:

Thevenin:				
R_{th}				
Obs.	Calculated			
582 Ω	585.092 Ω			
V_{th}				
Obs.	Calculated			
5.01	8.543			
Norton				
I_N	$R_{Ncal.}$	Obs.		
8	585.0982	582		

$V_L(V)$	$I_L(mA)$	$R_L(\Omega)$	$P(mW)$	
2.046	5	383	10.23	
2.088	5	403	10.44	$P_{max.}$
2.146	4.95	423	10.62	$P_{obs.}$ Cal
2.202	5	443	11.01	10.78 10.68
2.246	5	463	11.23	
2.275	5	483	11.375	
2.360	4.75	503	11.21	
2.405	4.6	523	11.063	
2.451	4.5	543	11.029	
2.497	4.4	563	10.987	

EXPERIMENT NO.: 3

DATE: 20 / 06 / 2022

Verification of Thevenin's, Norton's, and Maximum Power Transfer Theorem

AIM:

To verify Thevenin's, Norton's, and Maximum Power Transfer Theorem for the given circuit by circuit implementation on breadboard and using simulator.

APPARATUS AND COMPONENTS REQUIRED:


Resistors, DC Voltage source, Ammeter, DMM, breadboard, connecting wires, Sequel Simulator

THEORY:

Thevenin's Theorem:

Thevenin theorem is an analytical method used to change a complex circuit into a simple equivalent circuit consisting of a single resistance in series with a source voltage. Thevenin's Theorem states that "Any linear circuit containing several voltages and resistances can be replaced by just one single voltage in series with a single resistance connected across the load". In other words, it is possible to simplify any electrical circuit, no matter how complex, to an equivalent two-terminal circuit with just a single constant voltage source in series with a resistance (or impedance) connected to a load as shown below. Thevenin's Theorem is especially useful in the circuit analysis of power or battery systems and other interconnected resistive circuits where it will have an effect on the adjoining part of the circuit.

Thevenin's equivalent circuit:

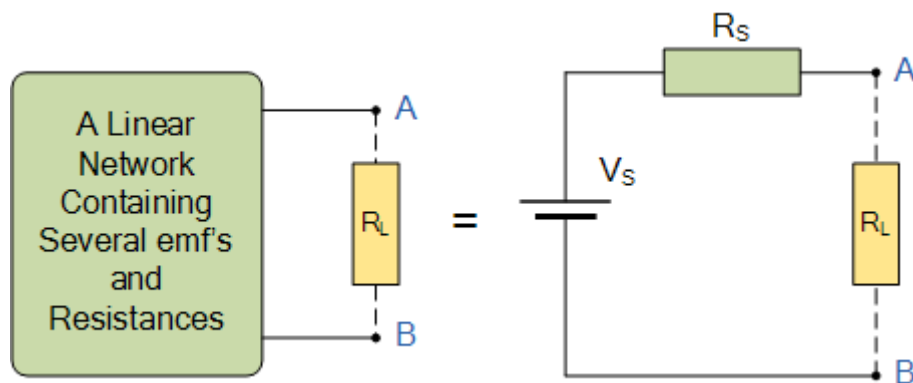


Norton's Theorem:

Norton's theorem is an analytical method used to change a complex circuit into a simple equivalent circuit consisting of a single resistance in parallel with a current source. Norton's Theorem states that "Any linear circuit containing several energy sources and resistances can be replaced by a single Constant Current generator in parallel with a Single Resistor".

As far as the load resistance, R_L is concerned with this single resistance, R_S is the value of the resistance looking back into the network with all the current sources open-circuited and I_S is the short circuit current at the output terminals as shown below.


Norton's equivalent circuit:

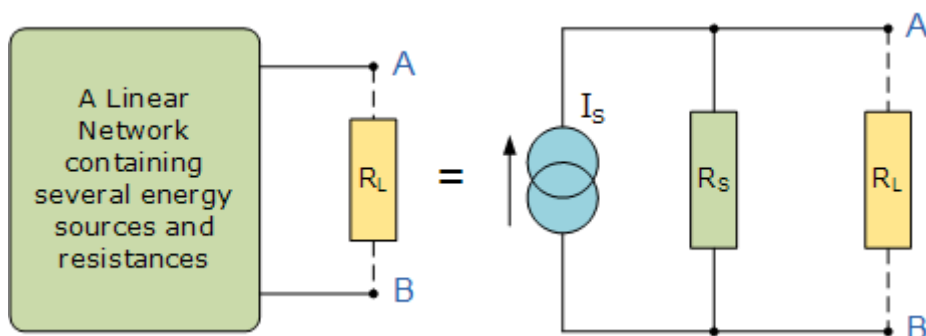

Maximum Power Transfer Theorem:

Maximum Power Transfer Theorem explains that to generate maximum external power through a finite internal resistance (DC network), the resistance of the given load must be equal to the resistance of the available source.

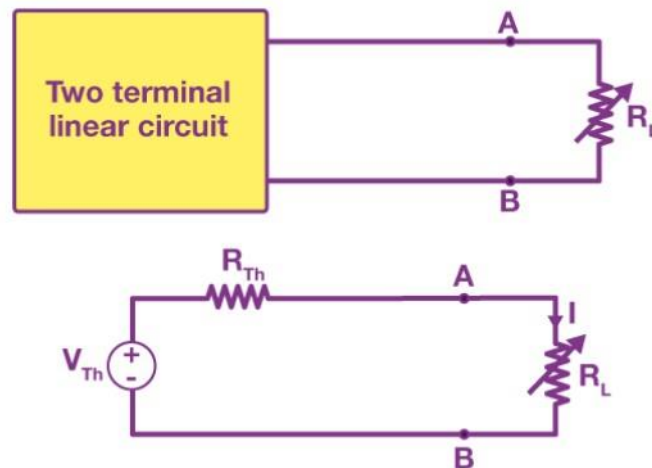In other words, the resistance of the load must be the same as Thevenin's / Norton's equivalent resistance.



The fundamental Maximum Power Transfer formula is:


$$P_{\max} = V_{Th}^2 / 4R_{Th}$$

$$\begin{aligned} \frac{dP}{dR_L} &= 0 \\ &= \frac{d}{dR_L} \left(\frac{V_0}{R_L + R_{Th}} \right)^2 R_L = 0 \\ &= \frac{d}{dR_L} \frac{V_0^2 R_L}{(R_L + R_{Th})^2} = 0 \\ &= \frac{(R_L + R_{Th})^2 \frac{d}{dR_L} (V_0^2 R_L) - V_0^2 R_L \frac{d}{dR_L} ((R_L + R_{Th})^2)}{(R_L + R_{Th})^4} = 0 \\ &= \frac{(R_L + R_{Th})^2 V_0^2 - V_0^2 R_L \times 2(R_L + R_{Th})}{(R_L + R_{Th})^4} = 0 \\ &= \frac{V_0^2 (R_L + R_{Th})(R_L + R_{Th} - 2R_L)}{(R_L + R_{Th})^4} = 0 \\ &= \frac{V_0^2 (R_L + R_{Th})(R_{Th} - R_L)}{(R_L + R_{Th})^4} = 0 \\ R_{Th} - R_L &= 0 \\ R_{Th} &= R_L \end{aligned}$$

Therefore, the value of $P_{\max} = I^2 R = [V_{Th} / (R_{Th} + R_L)]^2 * R_{Th} = V_{Th}^2 / 4R_{Th}$

PROCEDURE:



- 1) Connect the circuit as shown in the circuit diagram.
- 2) Keep the voltage such that the maximum current does not go beyond the range of the milliammeter.
- 3) Vary the load resistance from minimum to maximum.
- 4) Note the corresponding load current (I_L) and the voltage across the load V_L .
- 5) Calculate the power dissipated in the load resistance as $V_L * I_L$.
- 6) Plot the graph of P_L v/s R_L .
- 7) Obtain observed values of V_{Th} and R_{Th} and I_N
- 8) Implement the given circuit using Sequel Simulator.
- 9) Simulate the circuit, find V_{Th} , I_N and get the graph of P_L v/s R_L
- 10) Verify with the theoretical solution.

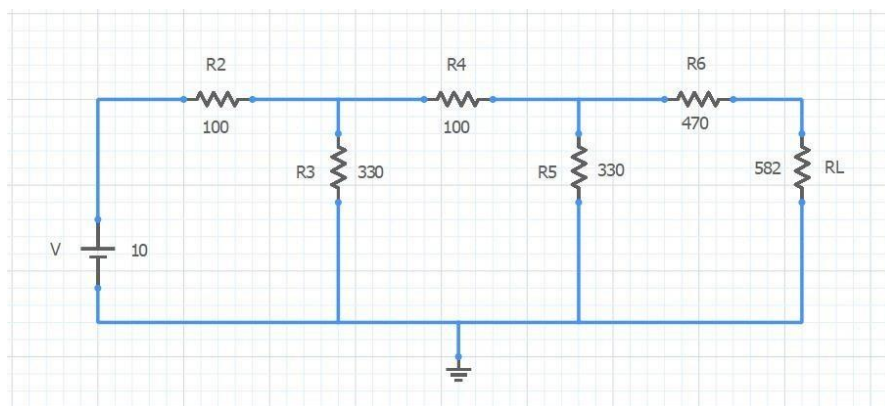RESULT:

	Variable	Value
1	V	2.492218e+000
2	I	4.282162e-003
3	P	1.067208e-002
4	R	5.820000e+002

V_{Th} (V)			$R_{Th} = R_N$ (Ω)			I_N (mA)			P_{max} (mW)		
Theoretical	Observed	By Simulation	Theoretical	Observed	By Simulation	Theoretical	Observed	By Simulation	Theoretical	Observed	By Simulation
5.00	5.01	5.00	585.098	582	585.098	8.543	8	8.543	10.68	10.78	10.68

GRAPH:

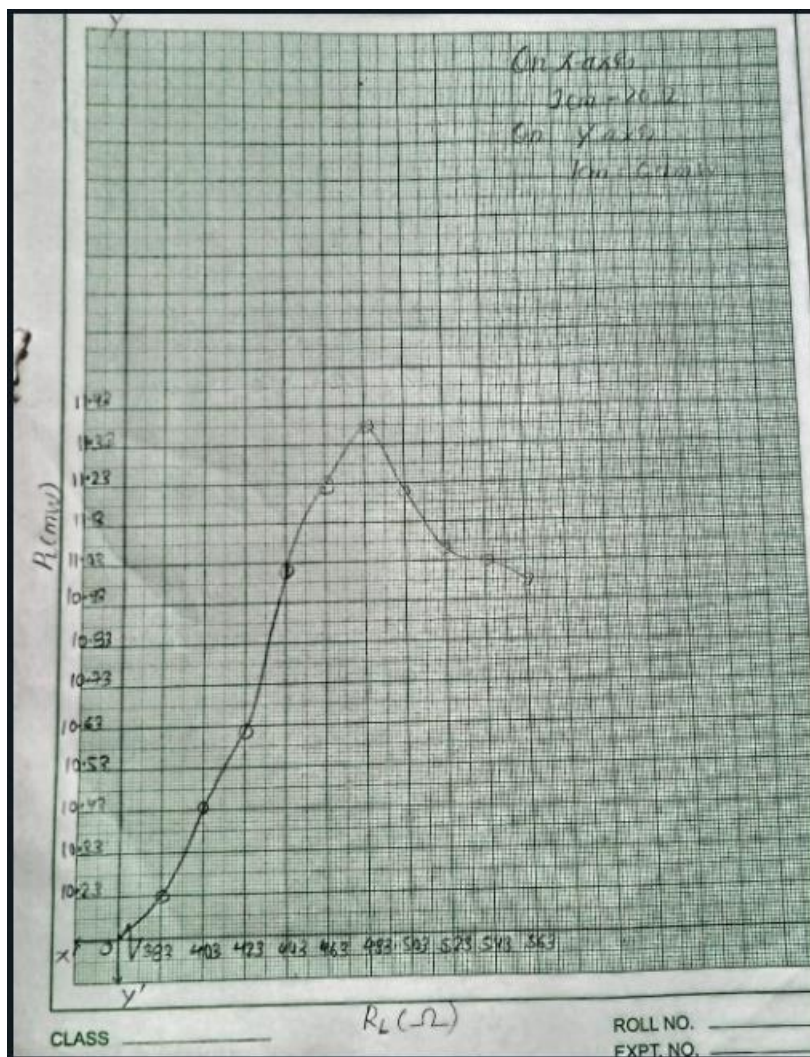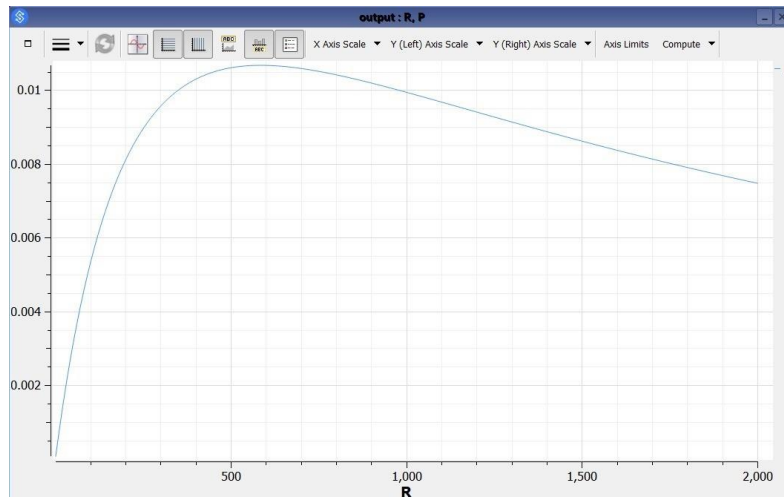

CONCLUSION:

In this experiment we learned about
Thevenin's, Norton, & Maximum Power transfer
theorem

We verified by implementing, calculating
and simulating on sequel.

We also plotted a graph.