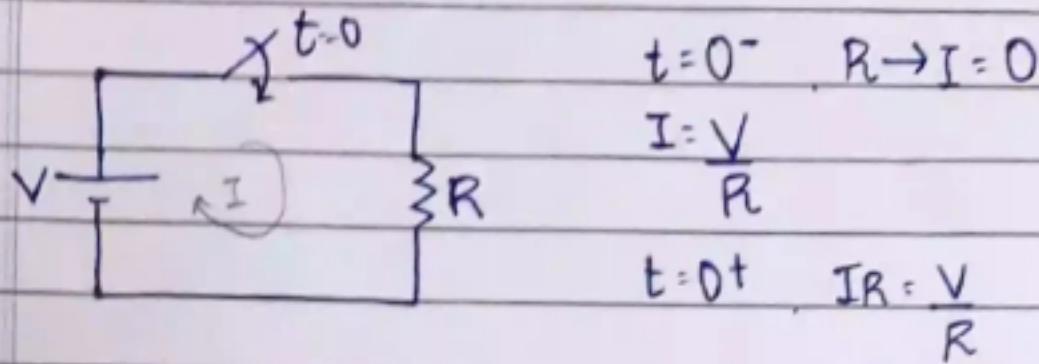


Lhp : TRANSIENT ANALYSIS

1. BEHAVIOR OF RESISTOR:




$$t = 0^- \quad R \rightarrow I = 0$$

$$I = \frac{V}{R}$$

$$t = 0^+ \quad IR = \frac{V}{R}$$

2. BEHAVIOR OF INDUCTOR:

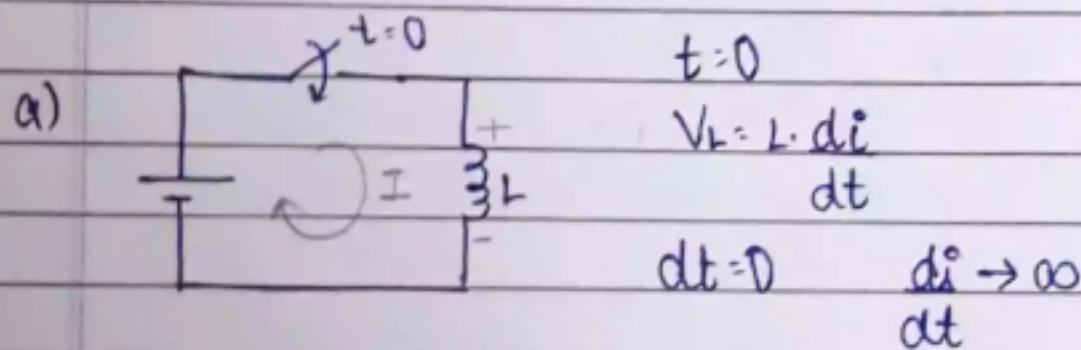

$$t = 0$$

$$V_L = L \cdot \frac{di}{dt}$$

$$dt = 0 \quad \frac{di}{dt} \rightarrow \infty$$

$V_L \rightarrow \infty$ practically not possible


Inductor opposes the instantaneous change of current

$$t = 0^- \Rightarrow t = 0^+$$

$$i_{LC0^-} \Rightarrow i_{LC0^+} = 0$$

At $t = 0^+ \Rightarrow$ Open Circ.

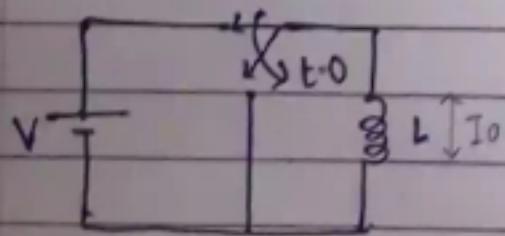b) If a voltage is applied across the inductor continuously.



At $t = 0$ voltage source is removed

$$t = 0^- \rightarrow I_0$$

$$t = 0^+ \rightarrow I_0$$

During transition it will act as a current source with I_0 current


$$I_{LC0+} = I_{LC0-} = I_0$$

$$V_L = L \cdot \frac{di}{dt}$$

$t = \infty$. no change in current

$$\therefore V_L = 0 \Rightarrow \text{Short Circuited}$$

c)

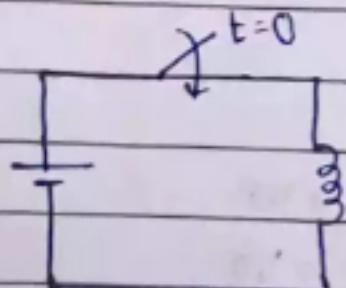 $t = \infty$


$$V_L = L \cdot \frac{di}{dt} = 0$$

$$\frac{di}{dt} \rightarrow 0$$

 $t = \infty \Rightarrow \text{O.C.}$

$t = 0$	$t = 0+$	$t = \infty$
$\xrightarrow{\text{L}}$	$\xrightarrow{\text{o.c}}$	$\xrightarrow{\text{s.c}}$
$\xrightarrow{\text{I}_0}$	$\xrightarrow{I_0}$	$\xrightarrow{I_0}$

3. (b) BEHAVIOUR OF CAPACITOR.

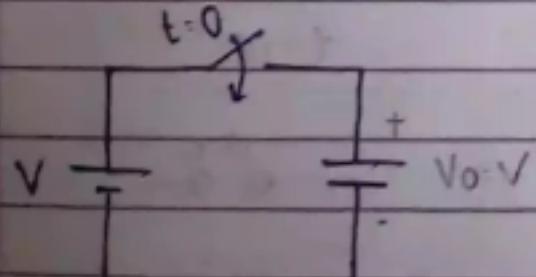

$$Q = CV$$

$$\frac{dQ}{dt} = C \cdot \frac{dV}{dt}$$

$$i_C = C \cdot \frac{dV}{dt}$$

$$dt \rightarrow 0, \frac{dV}{dt} \rightarrow \infty$$

$$\therefore i_C \rightarrow \infty$$


Capacitor opposes instant change of voltage.

$$t=0^- \rightarrow t=0^+$$

$$\downarrow 0$$

$$V_{CC0^+} = 0$$

b) Voltage is applied continuously.

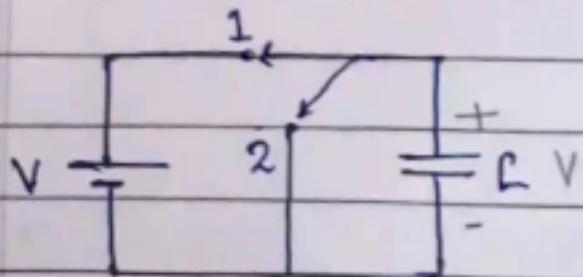

$$t=0^+$$


$$t=0^- \rightarrow V_{CC0^-} = V_0$$

$$t=0^+ \rightarrow V_{CC0^+} = V_0$$

$$i = C \cdot \frac{dv}{dt} \quad i_C = 0$$

$$t=\infty, i_C = 0 \quad O.C.$$

c)

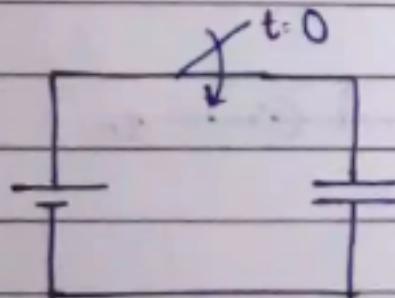

$$t=\infty$$

$$i = C \cdot \frac{dv}{dt} = 0$$

$$i_C = 0 \Rightarrow O.C.$$


Initial

Final

$$t=0$$


$$t=0^+$$

$$t=\infty$$

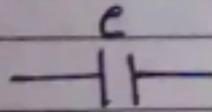

S.C.

O.C.

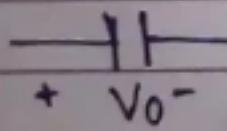

$$V_0^-$$

O.C.

LINEAR DIFFERENTIAL EQUATION


$$\frac{di}{dt} + PI = Q$$

$P \rightarrow \text{const}$



$Q \rightarrow \text{Forced excitation}$

- AC
- DC
- Any other

$$\text{SOLN: } PI + CF$$

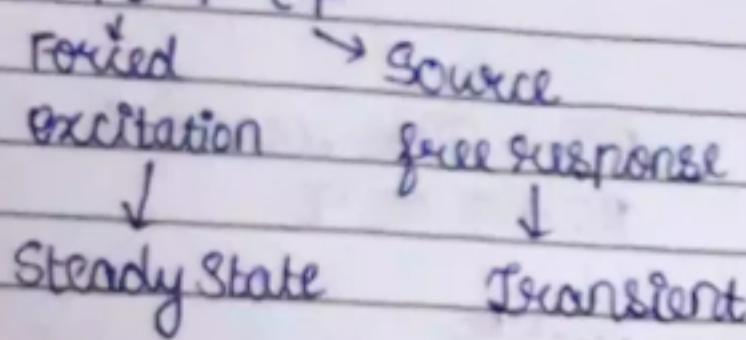

→ SOURCE FREE RESPONSE OF RC CIRCUIT.

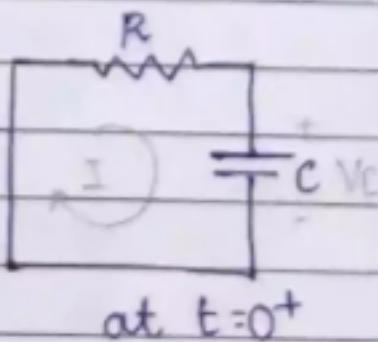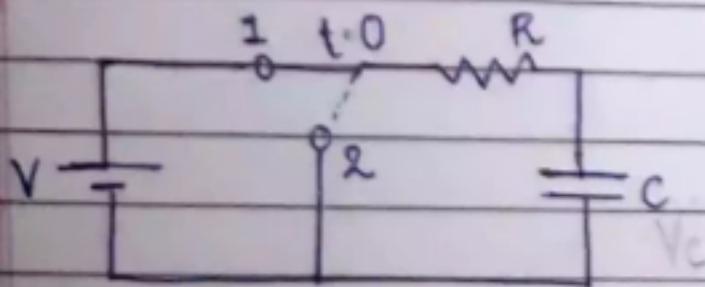

$$t=0^-, V_c = V$$

$$t=0^+, V_c = V$$

$$-IR - V_c = 0$$

$$IR + V_c = 0$$

$$R \left[C \cdot \frac{dV_c}{dt} \right] + V_c = 0$$

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = 0 \quad (\because \frac{di}{dt} + PI = 0)$$

§ No force eqⁿ: $\rightarrow \dot{Q} = 0$

C·F only PI = 0

$$\frac{dV_C}{dt} + \frac{1}{RC} V_C = 0$$

$$\frac{di}{dt} + PI = 0$$

$$C \cdot F \rightarrow Ae^{-Pt}$$

$$V_C(t) = Ae^{-t/RC}$$

$$V_C(0^+) = Ae^0$$


$$V_C(0^+) = A$$

$$V = A$$

$$V_C(t) = Ve^{-\frac{t}{RC}}$$

RC \rightarrow Time constant

RC $\rightarrow T$ or T

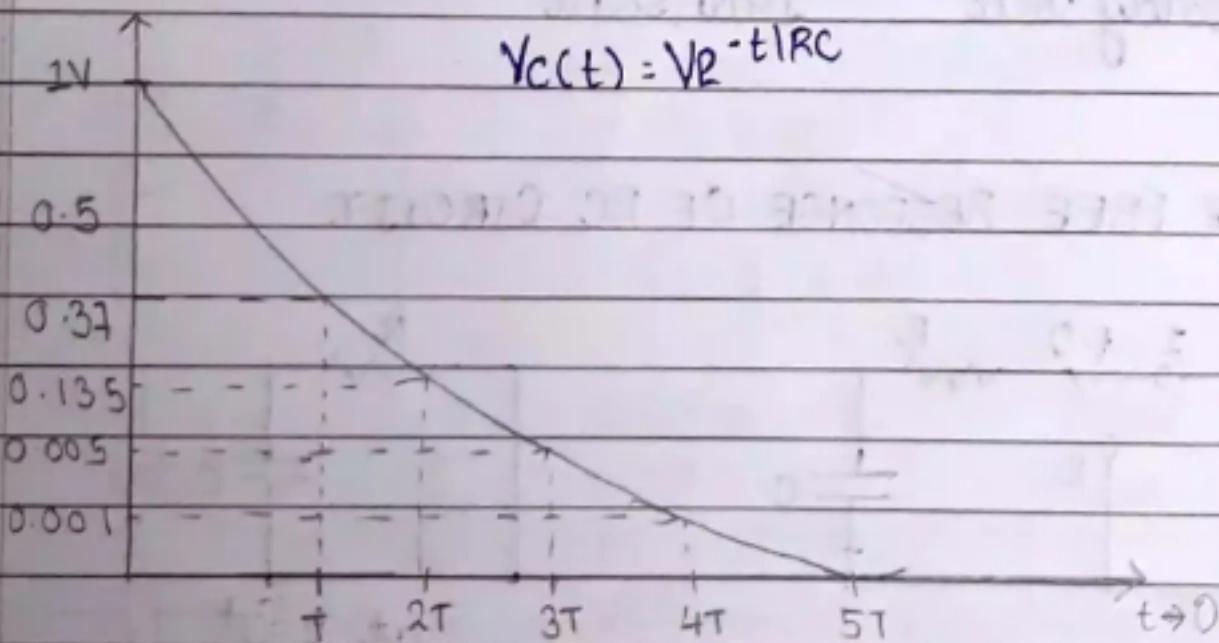

$$1T = 0.366V$$

$$2T = 0.135V$$

$$3T = 0.005V$$

$$4T = 0.001V$$

$$5T = 0.0007V$$


For eg if we want cap to get discharged in
 $5\mu s \rightarrow 5RC$

$$RC \rightarrow 1\mu s$$

$$R = 1k\Omega$$

$$C = \frac{1\mu s}{1k\Omega} = 10^{-9} F$$

→ SOURCE FREE RESPONSE OF RL CIRCUIT

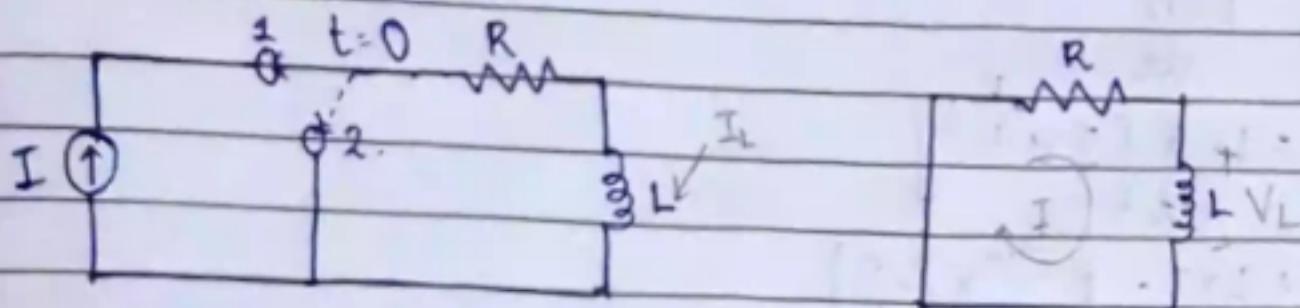

$$\text{at } t=0^-, I_L = 0$$

$$t=0^+, I_L = 0$$

Applying KVL,
 $\frac{dI}{dt}$

$$-iR - VL = 0$$

$$iR + L \frac{di}{dt} = 0$$

$$\frac{di}{dt} + \frac{R}{L}i = 0 \quad (\because \frac{di}{dt} + pi = 0)$$

$$i(t) = Ae^{-\frac{Rt}{L}}$$

$$I_L = i \text{ at } t = 0^+$$

$$i(0^+) = Ae^0$$

$$i(0^+) = A$$

$$i(t) = Ae^{-\frac{Rt}{L}} = A e^{-\frac{R}{L}t}$$

$$\tau = RL$$

$\frac{L}{R}$ - same constant = T ,

$$I(t) = I e^{-\frac{R}{L}t} = I e^{-t/T}$$

$$T \text{ or } T = \frac{L}{R}$$


→ Inductor voltage

$$V_L = L \cdot \frac{di}{dt}$$



$$= L \cdot \frac{d}{dt} [I e^{-\frac{R}{L}t}]$$

$$= L \times I \cdot e^{-\frac{R}{L}t} \times \left(-\frac{R}{L}\right)$$


$$V_L = -IR e^{-\frac{R}{L}t}$$

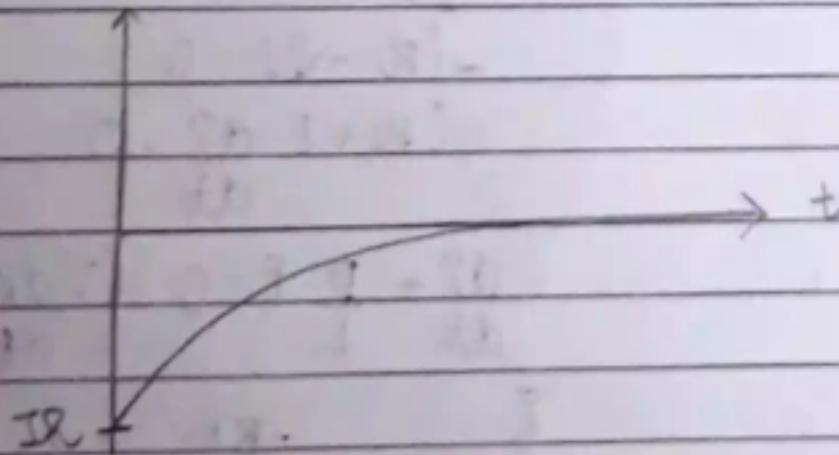

→ FORCED RESPONSE OF RC CIRCUIT

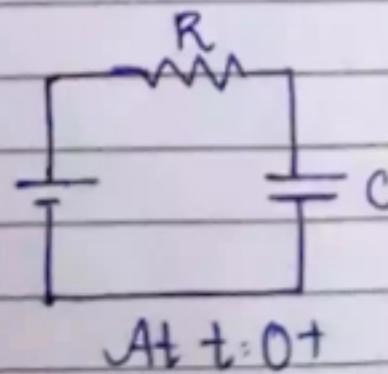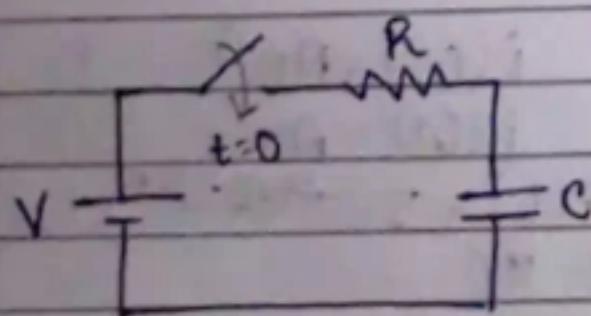

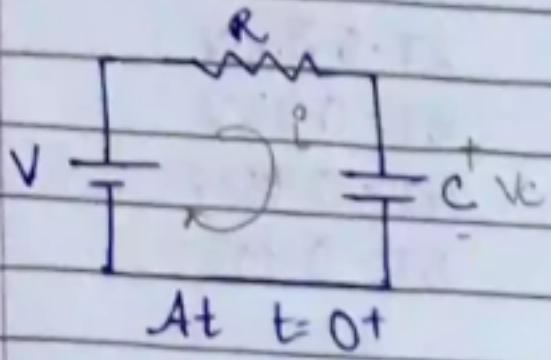At $t = 0^-$; $V_C = 0$
 $t = 0^+$; $V_C = 0$



Applying KVL

$$V - iR - V_C = 0$$

$$V = iR + V_C$$

$$V = R \left[C \cdot \frac{dV_C}{dt} \right] + V_C$$

$$\frac{dV_C}{dt} + \frac{1}{RC} V_C = \frac{V}{RC}$$

$$\frac{di}{dt} + PI = Q$$

$$P = \frac{1}{RC}, Q = \frac{V}{RC}$$

Solⁿ: P.I + C.F

$t \rightarrow \infty$ \downarrow SOURCE FREE

P.I $\rightarrow V_C(t \rightarrow \infty)$, $V_C = V$

$$P.I = V$$

$$C.F \rightarrow A e^{-Pt}, P = \frac{1}{RC}$$


$$= A e^{-\frac{1}{RC}t}$$

$$V_C(t) = V + A e^{-\frac{t}{RC}}$$

$$V_C(0^+) = V + A e^0$$

$$V_C(0^+) = V + A \Rightarrow 0 = V + A \therefore A = -V$$

$$V_c(t) = V - VR^{-t/RC}$$

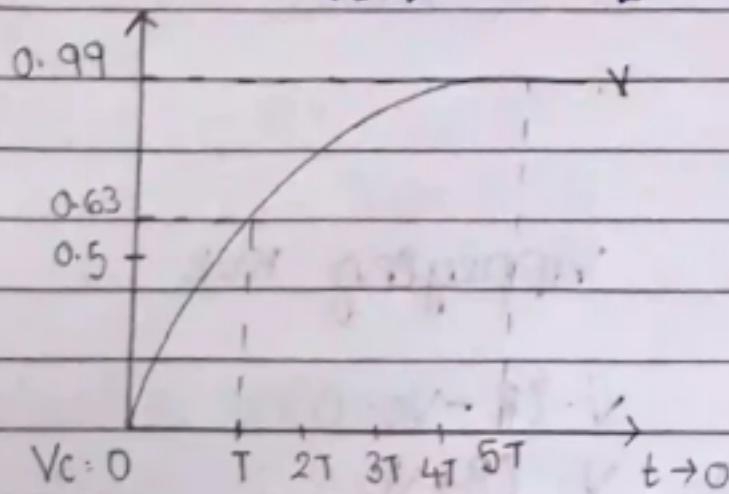

$$1T = 0.63V$$


$$2T = 0.865V$$

$$3T = 0.95V$$

$$4T = 0.982V$$


$$5T = 0.993V$$

→ FORCED RESPONSE FOR RL CIRCUIT

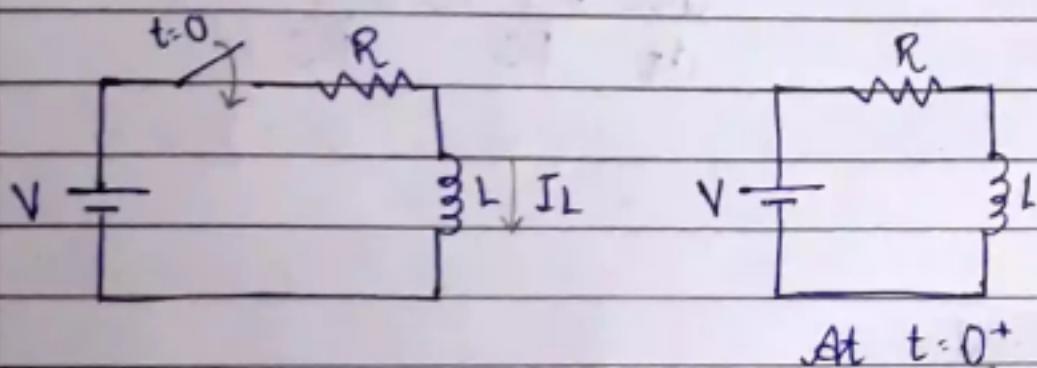

At $t = 0^-$, $I_L = 0$

At $t = 0^+$; $I_L = 0$

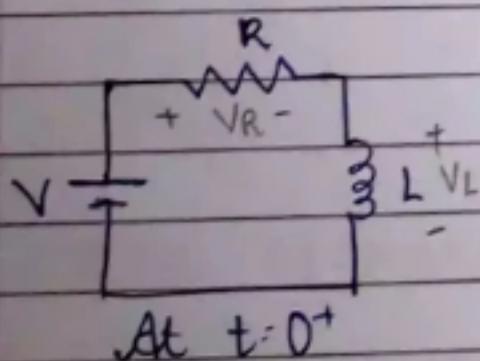

Applying KVL

$$V = VR + VL$$


$$= iR + L \frac{di}{dt}$$

$$\frac{di}{dt} + Ri = \frac{V}{L}$$

$$P = \frac{R}{L}, Q = \frac{V}{L}$$

SOLⁿ: P.T + C.F
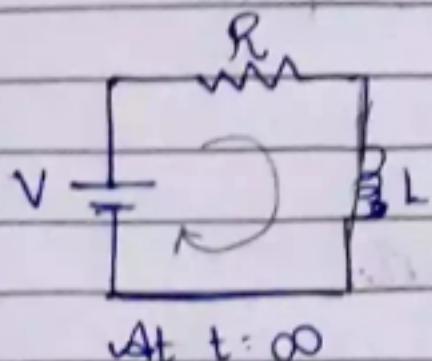
$$t \rightarrow \infty \quad \downarrow Q = 0$$



At Steady state \rightarrow Shunt circuit

$$\text{P.T} = I_L(t=\infty)$$

$$I_L = \frac{V}{R}$$

$$\text{P.I} = \frac{V}{R}$$

$$\text{C.F.} : A e^{-Pt}$$


$$A e^{-\frac{R}{L}t}$$

$$i(t) = \frac{V}{R} + A e^{-\frac{R}{L}t}$$

$$i(0^+) = \frac{V}{R} + A \quad \Rightarrow \quad A = -\frac{V}{R}$$

0
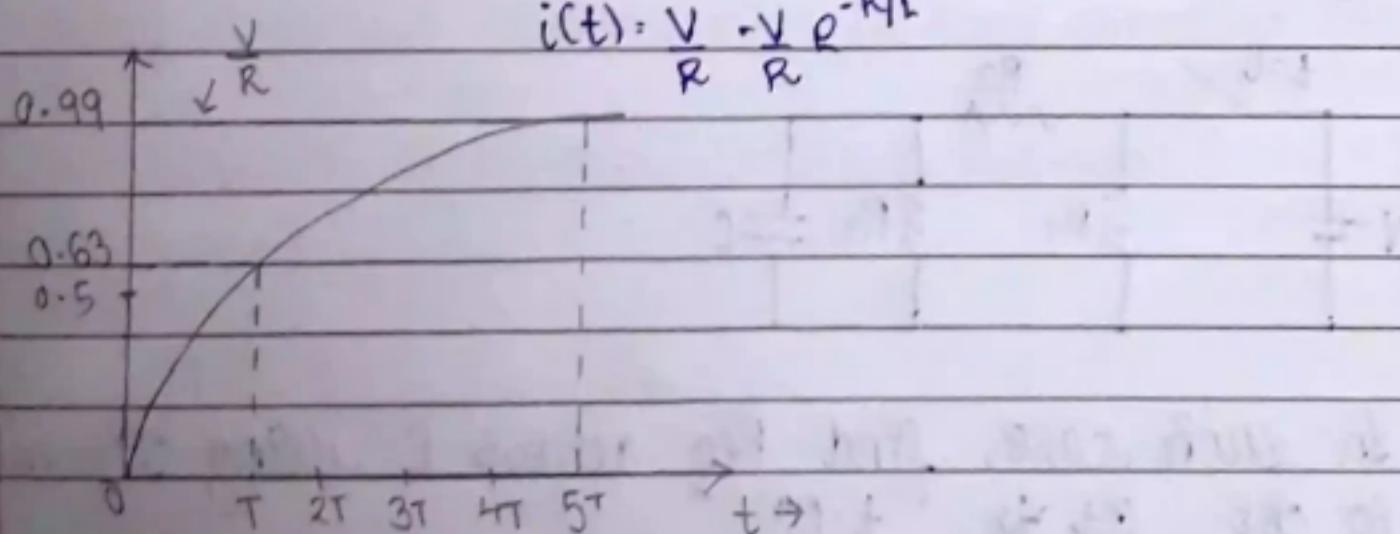
$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-\frac{R}{L}t}$$



$$1. V_C(t) = V - V_p e^{-t/RC} : \text{Forced excitation}$$

$$2. V_C(t) = V_p e^{-t/RC} : \text{Source free response}$$

$$3. i_L(t) = I_p e^{-Rt/L} : \text{Source free}$$

$$4. P_L(t) = \frac{V}{R} - \frac{V_p}{R} e^{-Rt/L} : \text{Forced input.}$$

$$1. V_C(t) \text{ or } = [\text{Final value}] + [\text{Initial - Genal}] e^{-t/T}$$

$$i_L(t) \quad t \geq 0$$


$$= V + [0 - V] e^{-t/T}, T = RC$$

$$= V - V_p e^{-t/RC}$$


$$\text{Source Free: } [0] + [V - 0] e^{-t/T}$$

$$= V e^{-t/RC}$$

If there are more than 1 elements.

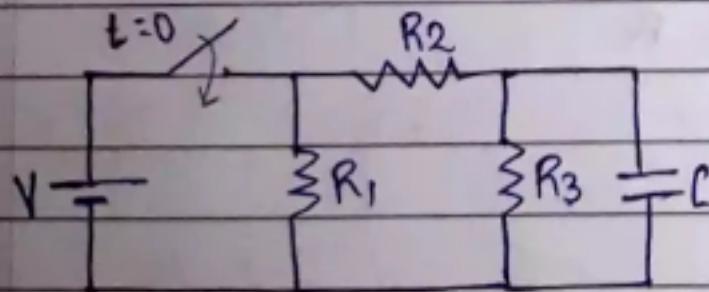

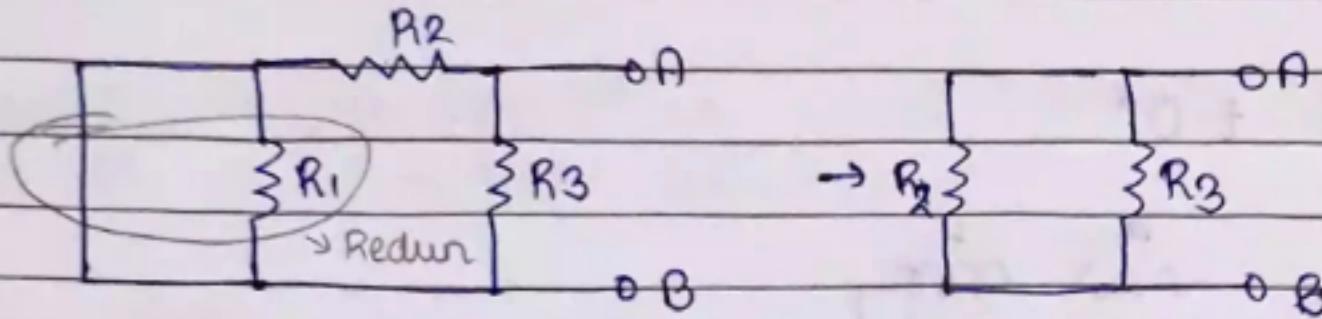In such case, find Req across C using Thevenin's eq ckt at $t=0^+$



$$\therefore R_{eq} = R_2 \parallel R_3$$

$$\therefore T \text{ or } \tau = RC$$

$$= R_{eq} \times C$$

$$= \left(\frac{R_2 \cdot R_3}{R_2 + R_3} \right) \times C$$

* IN SHORT 1 STEPS

1. Draw the circuit at $t=0^+$
2. Find initial conditions: $V_c(0^+)$ or $I_L(0^+)$
3. Find R_{eq} & (C_{eq} or L_{eq}) of ckt.
Time constant (τ) = $R_{eq} \times C_{eq}$
 $(\tau) = \frac{R_{eq}}{C_{eq}}$
4. Find final values of V_c or I_L (at time $\rightarrow \infty$)
5. Find solution: P.I + C.F
6. Total solution = Final value + (Initial - Final) $e^{-t/\tau}$