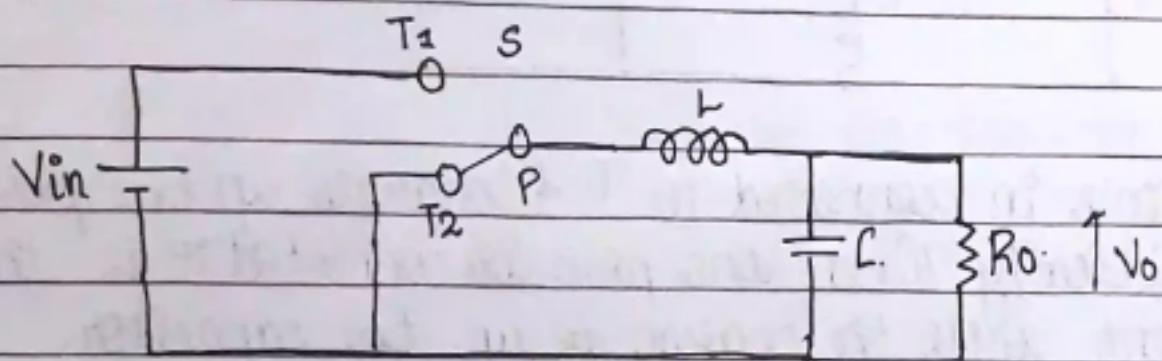


POWER CONVERTORS:-

BUCK CONVERTORS


→ Ckt diagram:

Buck converters



The energy is flowing from V_{in} to V_o . V_{in} is the higher voltage side, and V_o is lower.


Boost converters

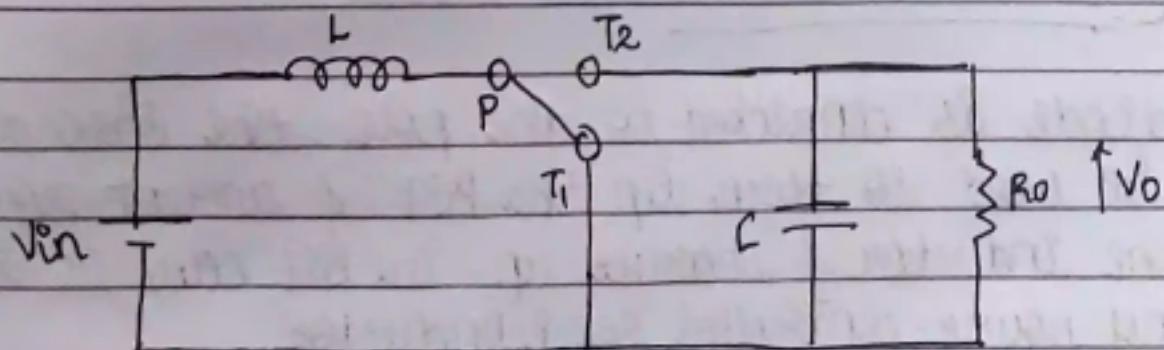

When pole is connected to T_1 , the inductor charges up. Pole is at 0 position. When pole is switched to T_2 , the inductor current cannot go to 0. The inductor will


discharge the magnetized current. Inductor current can't change suddenly. \therefore It is always connected to the pole.

Buck-boost converters

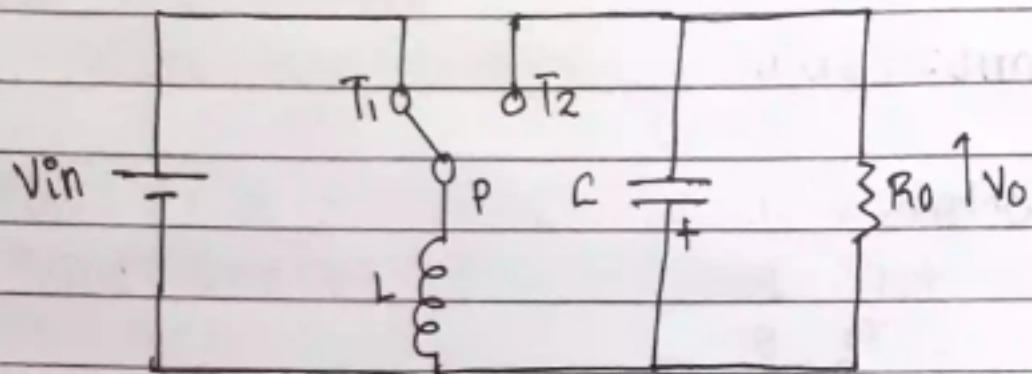

The pole is connected to T_1 & charges up the pole inductively. When the pole is connected to T_2 the current will charge up the capacitor.


→ Buck converter.

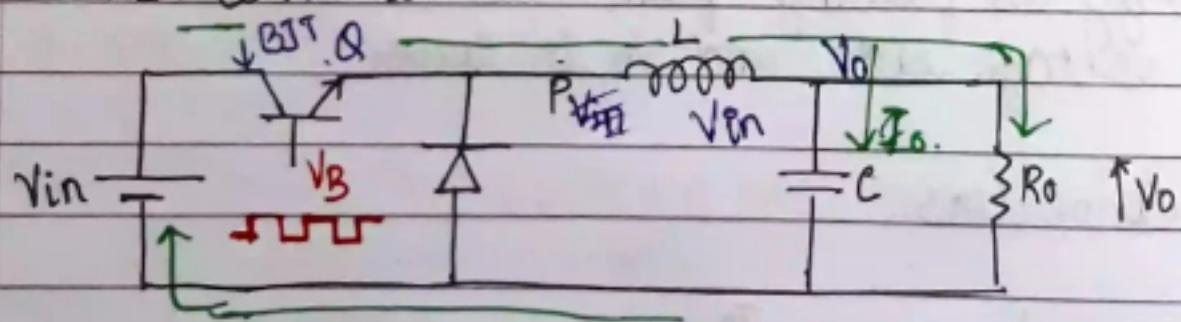

The diode is connected to the pole. The base drive will be used to turn on the BJT. If current flows the inductor & charges up. The BJT can be replaced by any power-controlled semiconductor.

$$d \Rightarrow \text{duty ratio} = \frac{T_{on}}{T_{on} + T_{off}}$$

$$d = \frac{T_{on}}{T_S}$$

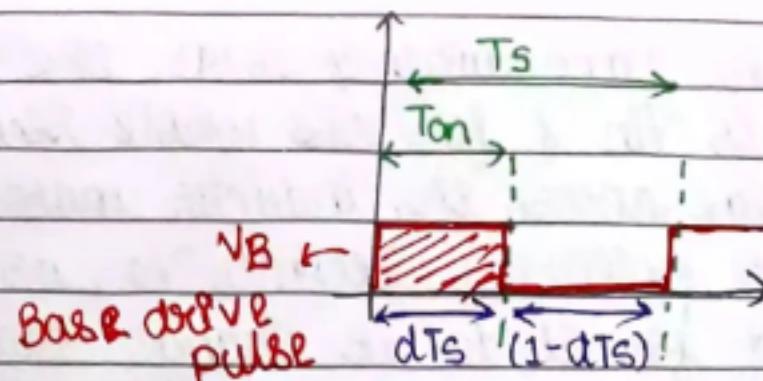

When $V_B \uparrow$ - Transistor ON

When $V_B \downarrow$ - Transistor off

When Q ON: $(V_{in} - V_o) dT_S$

When Q OFF: $-V_o (1-d) T_S$


These 2 must be balanced for inductor to work properly

$$(V_{in} - V_o) dT_S + -V_o (1-d) T_S = 0$$

$$V_{in} \cdot d = V_o (d+1-d)$$

$$V_o = V_{in} \cdot d$$

→ Boost converter

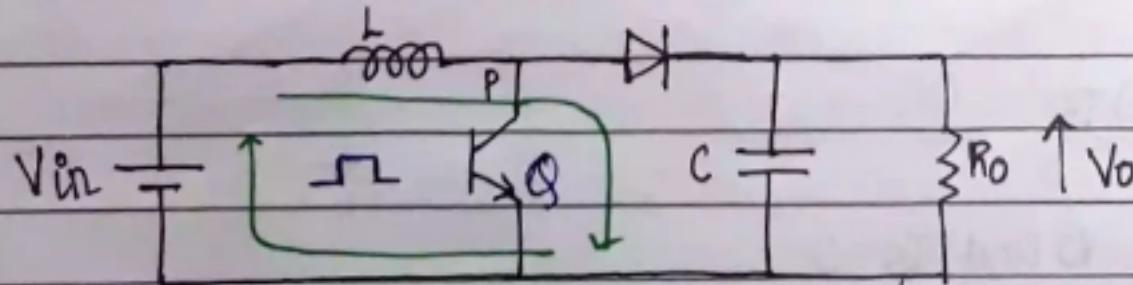

$$Q_{on} (dT_S) = V_{in} \cdot dT_S$$

$$Q_{off} (1-d) T_S = (V_{in} - V_o) (1-d) T_S = 0$$

$$V_{in} = V_o (1-d)$$

$$V_o = \frac{V_{in}}{1-d}$$

at $d=0$, Q is never on


at $d \rightarrow 1$, $V_o \uparrow$

During the time when Q is on, the potential across the inductor is V_{in} & for the whole second, the voltage or potential across the inductor must change sign. As the potential becomes V_o , as the diode is conducting, for it to be change sign $V_o \geq V_{in}$.

$V_o = V_{in}$ when $d=1$, transistor is not switching
 $\rightarrow d=1$ & it is continuously on. The diode is off.

The capacitor is decoupled from the circuit & eventually discharge from ckt. $\therefore d=1$ we should not take, but $d \rightarrow 1$

→ Buck-Boost Converter.

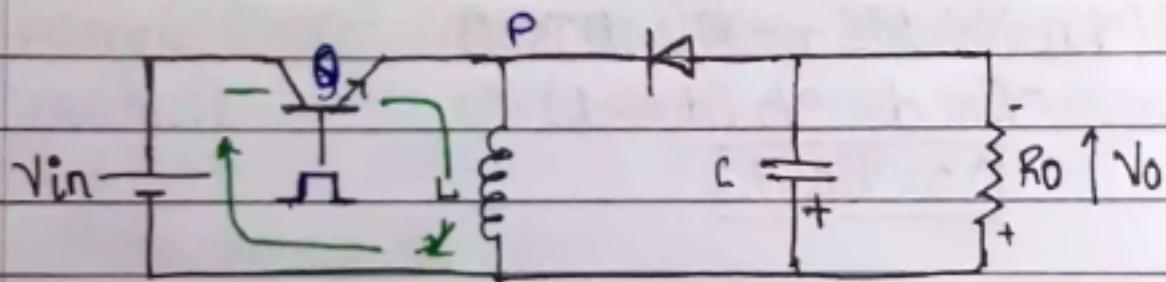

$$Q_{ON} : dT_s$$

$$Q_{OFF} : (1-d)T_s$$

$$V_{in} \cdot dT_s + V_o (1-d)T_s = 0$$

$$\boxed{V_o = -\frac{V_{in} \cdot d}{1-d}}$$




$$\text{at } d=0, V_o=0$$

$$\text{at } d=0.5, V_o = -V_{in}$$


$$\text{at } d > 0.5, V_o > |V_{in}| - \text{Boost}$$

$$\text{at } d < 0.5, V_o < |V_{in}| - \text{Buck}$$

⇒ BUCK- CONVERTOR

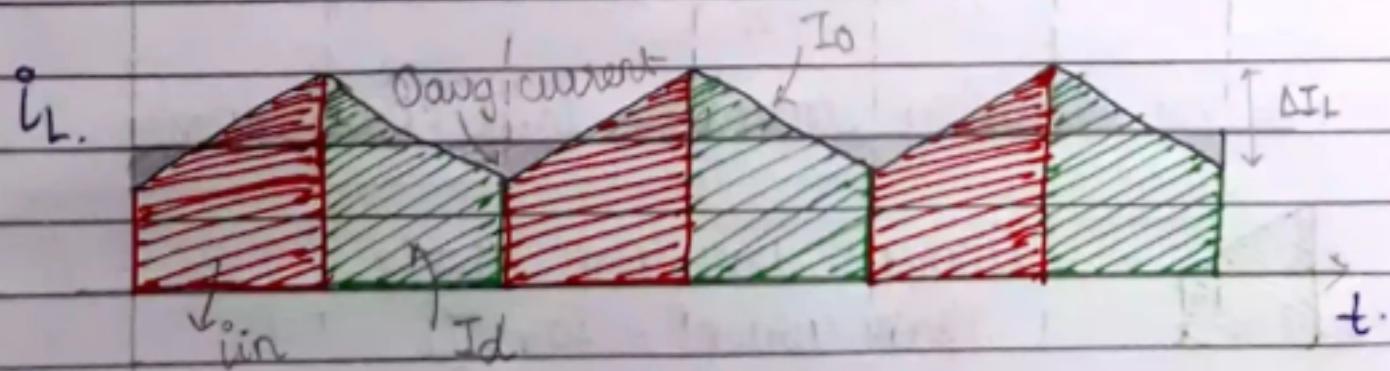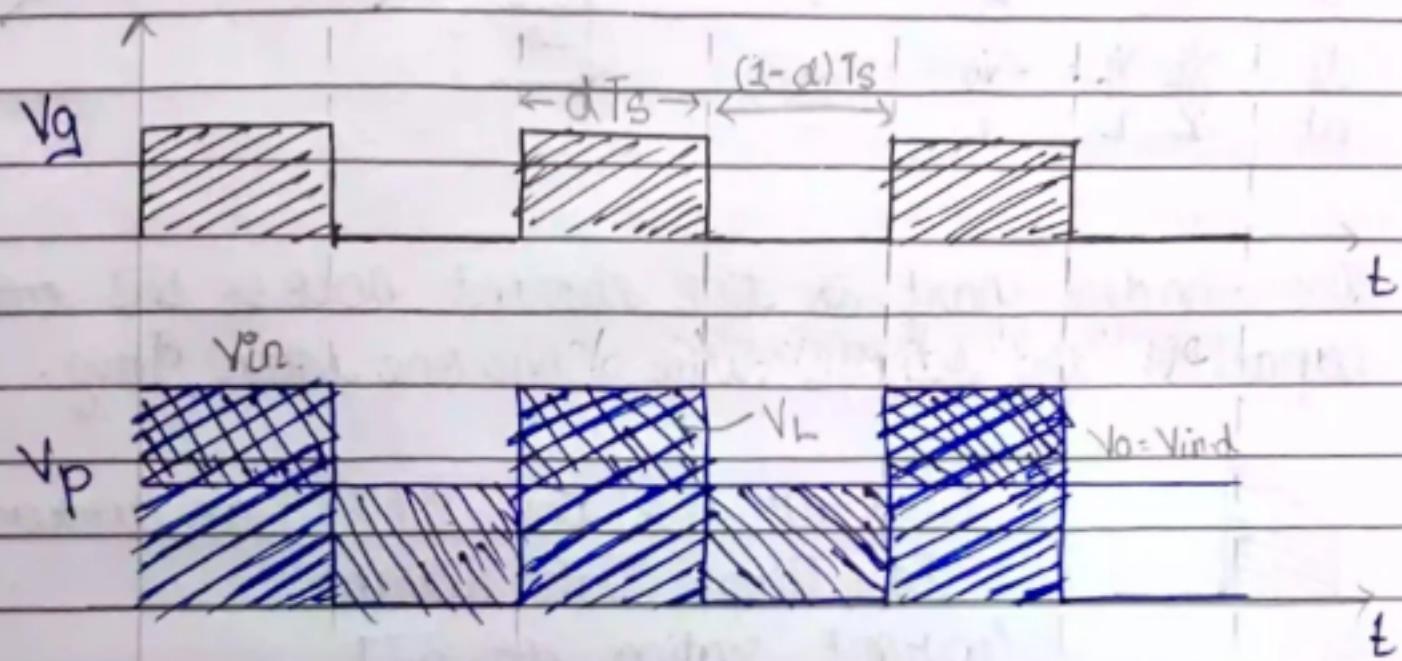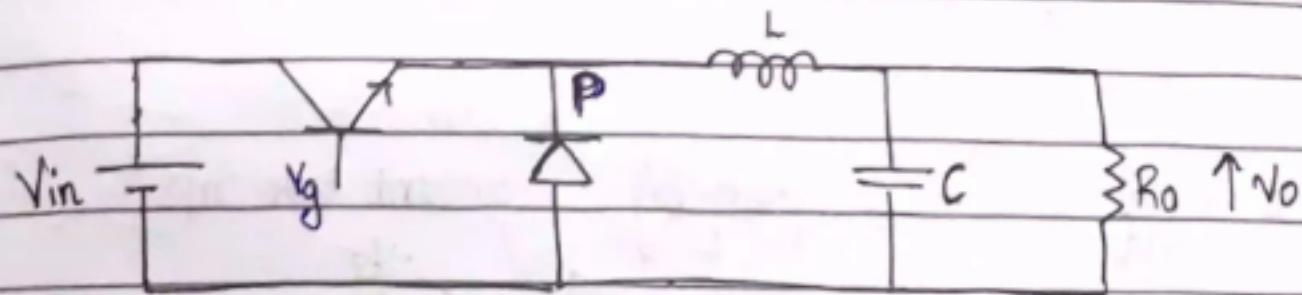

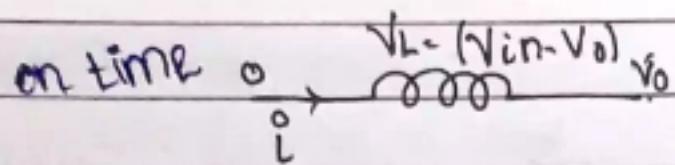When V_g is on, V_p will be V_{in} . When diode is off $\Rightarrow 0$
 When diode is on, the rest of circuit is free-wheeling & the
 P is connected to ground. \therefore The power withstand capacity
 of BJT or any power-controlled semi is V_{in}




$$V_L = L \cdot \frac{di}{dt}$$


$$\frac{di}{dt} = \frac{V_L}{L} = \frac{V_{in} - V_o}{L}$$

$$\frac{di}{dt} = \frac{V_L}{L} \quad V_L = -\frac{V_o}{L}$$

($V_{in} - V_o$) current thru. Cap.

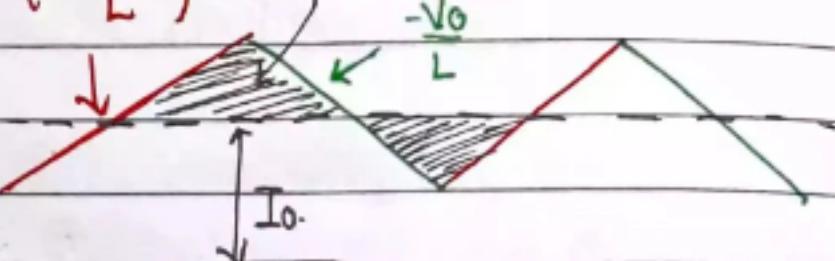

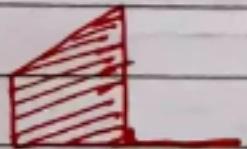The shaded part is the current across the current capacitor; the ripple value .. the one with $\frac{V_o}{L}$.




- Current thru the BJT: Peak current $I_o + \text{Ripple Peak current}$

Current rating for BJT

$$= I_o + \frac{\Delta I_L}{2} \text{ (Peak current)}$$


Avg current: $I_o \cdot d$ (Duty cycle)

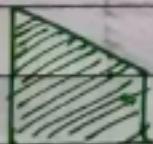

- Current thru the diode.

$$\text{Peak current} = I_o + \frac{\Delta I_L}{2}$$

Average value: $I_o \cdot (1-d)$

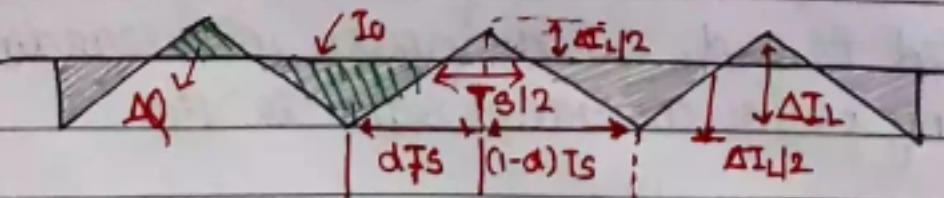

Current thru the capacitor

Green shaded parts should be equal

Area of Δ = Charge

$$\Delta Q = \frac{1}{2} \times b \times h$$

$$= \frac{1}{2} \times T_S \times \frac{\Delta I_L}{2}$$

$$= \frac{T_S \cdot \Delta L}{8} \Rightarrow \frac{\Delta I_L}{8 f_S}$$

$$\Delta Q = C \cdot \Delta V$$

$$= \frac{\Delta i_L}{8 f_S} \Rightarrow \boxed{C = \frac{\Delta i_L}{8 f_S \cdot \Delta V}}$$


ΔV = Ripple across capacitance

Δi_L = assumed in designing

10% of I_{max} (known)

f_S = Designing aspect (known)

Inductor : L

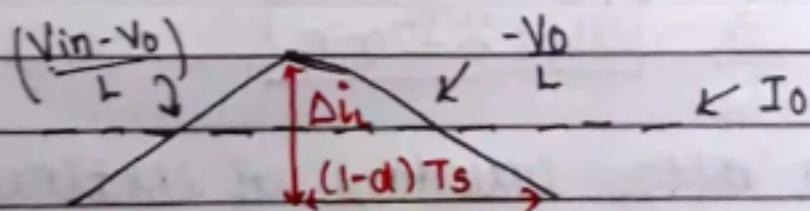

$$V_L = L \cdot \frac{di}{dt} \quad |V_o| = \frac{V_o}{L} = \frac{di}{dt} = \frac{\Delta i_L}{\Delta T} = \frac{\Delta i_L}{(1-d) T_S}$$

$$V_o = \frac{\Delta i_L}{L (1-d) T_S} \quad \text{OR} \quad L = \frac{V_o (1-d)}{\Delta i_L \cdot f_S}$$

$$I_{max} = V_o (1 - d_{min})$$

$$10\% \text{ of } I_{max} \quad \Delta i_L \cdot f_S$$


$$V_o = V_{in} \cdot d$$

$$d = \frac{V_o}{V_{in}} = \frac{V_o}{V_{in, max}} \quad \text{or} \quad \frac{V_o}{V_{in, min}}$$

These are the limiting values of d.

$$L = \frac{V_o}{f_s} (1-d)$$

$$\Delta i_L \cdot f_s$$

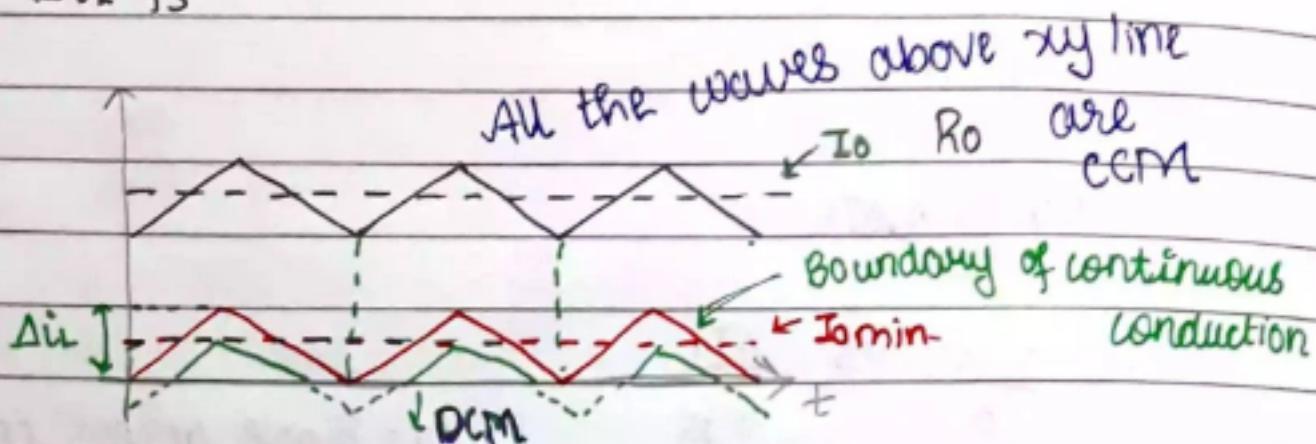


If $R_o \uparrow$ then $I_o \downarrow$. But $\Delta i_L \cdot f_s$ will not change
 i.e. the slopes will not change as they are dependent
 on $V_{in} - V_o$ & $\frac{V_o}{L}$ & independent of R_o . During limit, it
 will just touch the t-axis

$$\frac{\Delta i_L}{2} = I_{o\min} \Rightarrow \boxed{\Delta i_L = 2I_{o\min}}$$

Any wave form after boundary of continuous conduction appear like the green waveform. They are called discontinuous conduction mode, or DCM. We should ensure that the inductor operates in CCM. All the analysis are for CCM

\Rightarrow BOOST CONVERTER




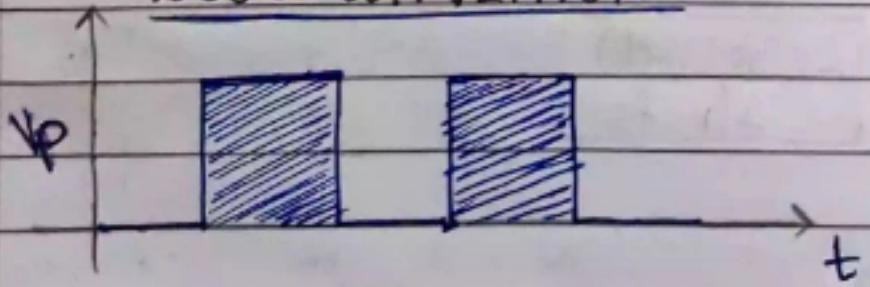


During time dT_s , diode is off, transistor is conducting
 Diode conducting capability = $V_o \cdot \epsilon$

When BJT is off, diode conducting.

\therefore BJT conducting capability = V_o (during off time)

→ BOOST - CONVERTOR.

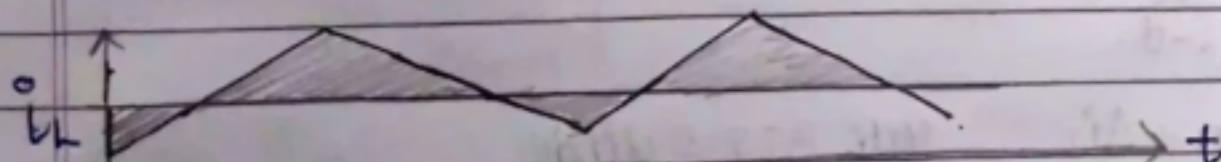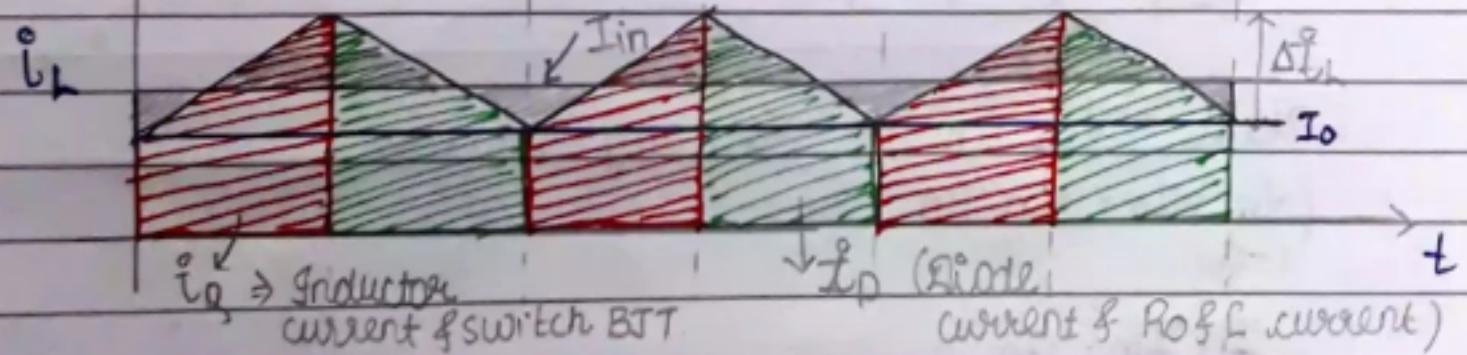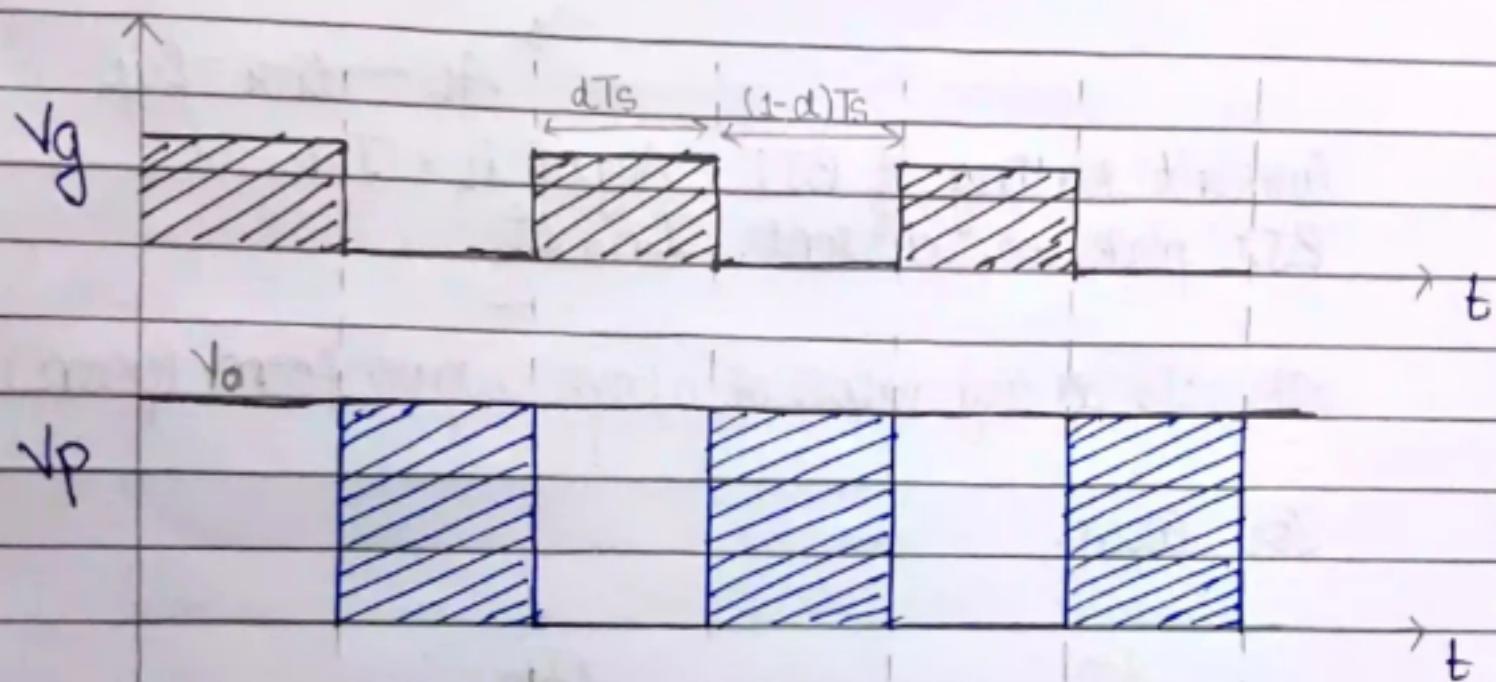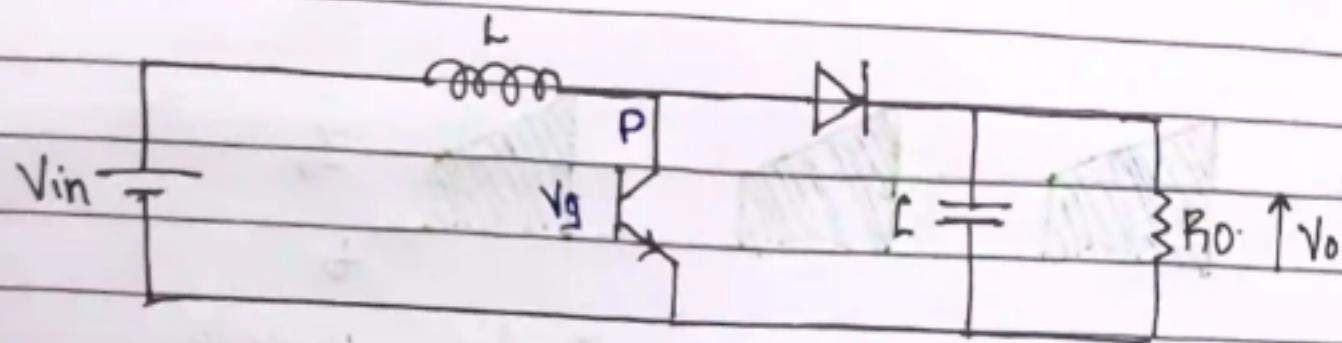

Rise in slope in switch is when transistor = ON. (V_{in})


Fall in slope

(output $V_{out} >$ input voltage)

Here the average current is indicating source current or I_{in} and not I_o as in buck converter.

diode = ON ($V_{in} - V_L$)

Digital current I_{in}

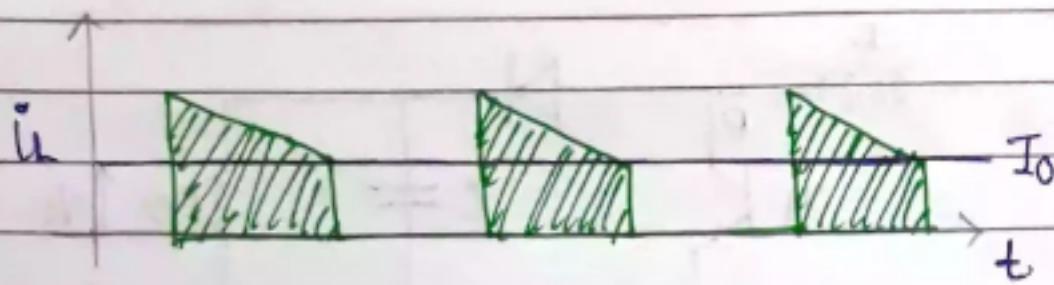

This will have 2 parts


- Avg - thru R_o
- AC - thru Cap.

Current rating of BJT : Avg of $i_L = I_{in}$

BJT peak current: $I_{in} + \frac{\Delta i_L}{2}$

~~∴~~ I_0 is avg value of above wave form (green).

For BOOST:

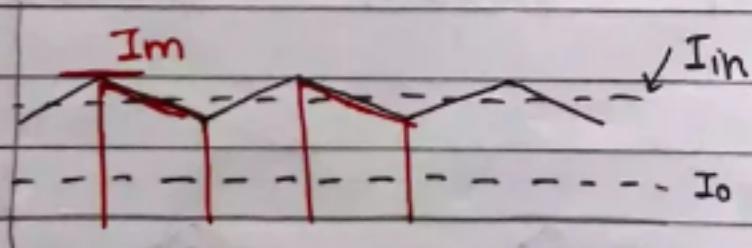

$\forall I_0 = V_{in} I_{in}$.. for any converter


$$\left(\frac{V_{in}}{1-d}\right) I_0 = V_{in} \cdot I_{in}$$

$$\therefore I_{in} I_{in} = \frac{I_0}{1-d}$$


$$I_{max} = I_{in} + \frac{\Delta i_L}{2} \quad \text{Rate BJT \& diode}$$

Diode \Rightarrow peak inverse rating $> V_o \quad \nexists V_p$

BJT $\Rightarrow V_{CEO} > V_o$

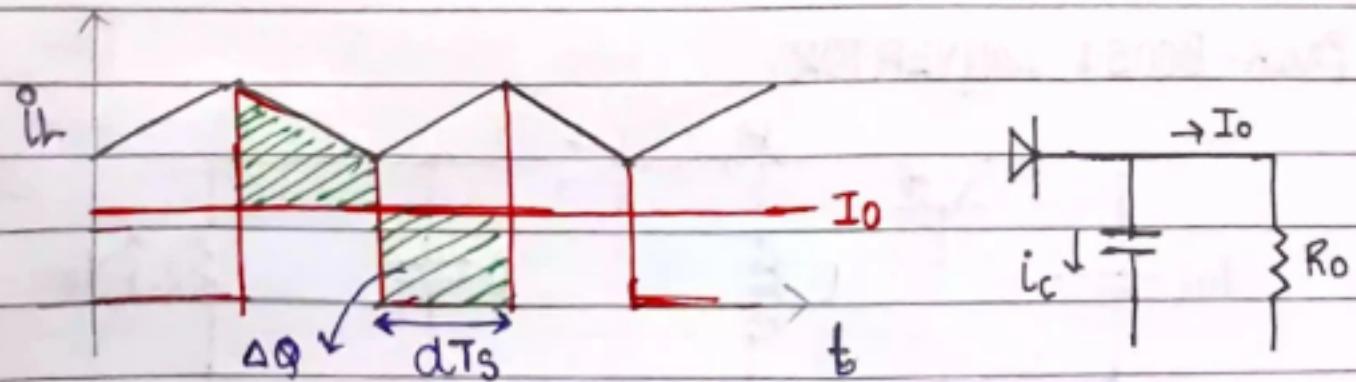

- ~~do~~ current thru diode

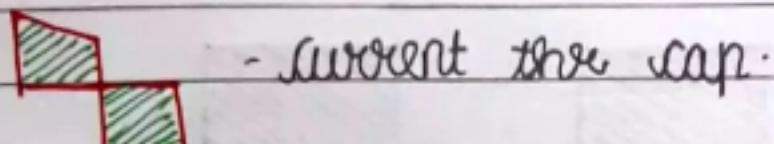


green areas should be equal

$$\text{Area} = \Delta Q = I_0 \cdot dT_s = CAV$$

$$L = \frac{I_0 \cdot d}{CAV \cdot fs}$$

Normally 10V is used
for AV.



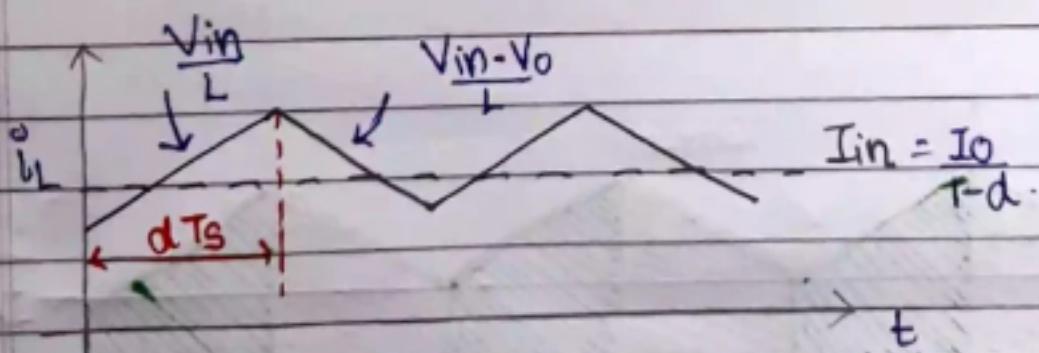


$$\frac{V_{in}}{L} = \frac{di_L}{dt} = \frac{\Delta i_L}{\Delta T} = \frac{\Delta i_L}{dT_s}$$


$$\therefore L = \frac{V_{in} \cdot d}{\Delta i_L \cdot fs}$$


$$V_o = \frac{V_{in}}{1-d} = \text{if } \frac{V_{in \max}}{1-d_{\min}} \text{ or } \frac{V_{in \min}}{1-d_{\max}}$$

⇒ Buck-Boost CONVERTOR.

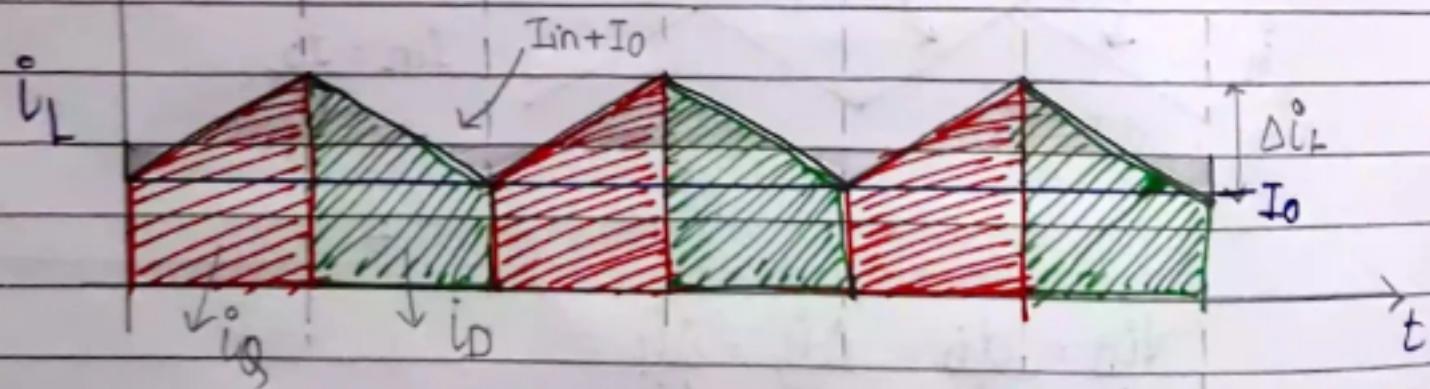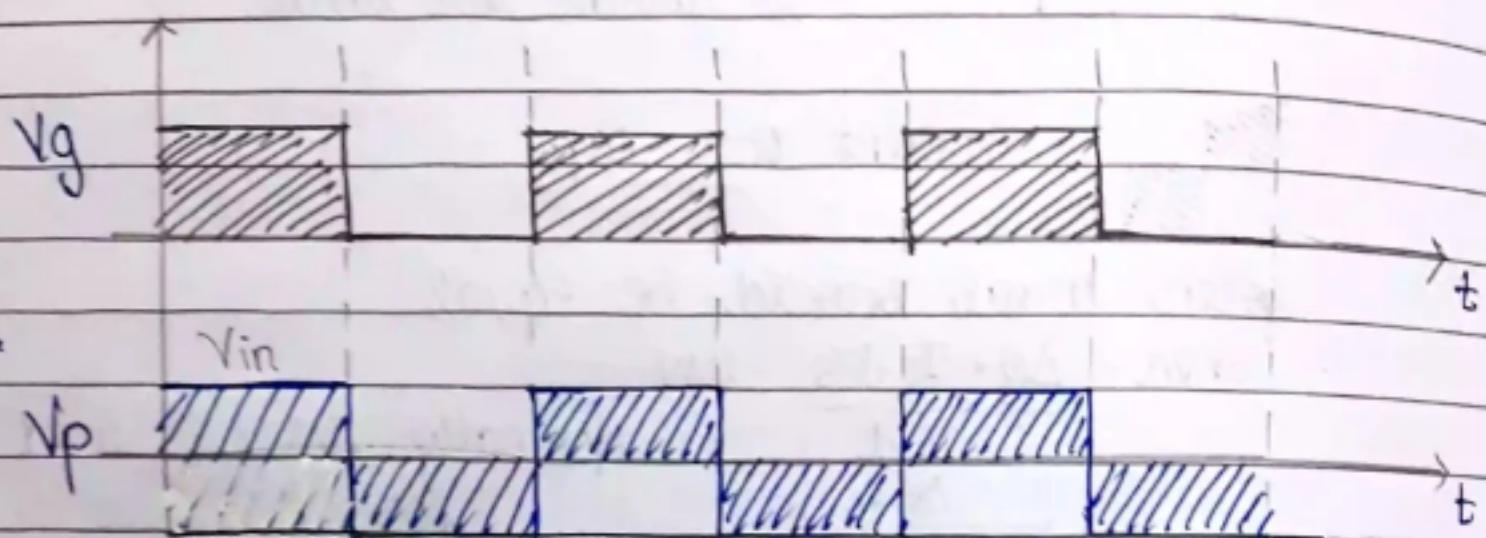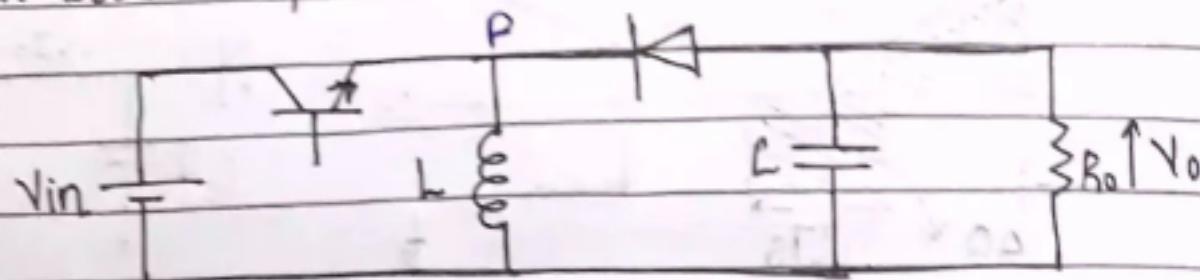

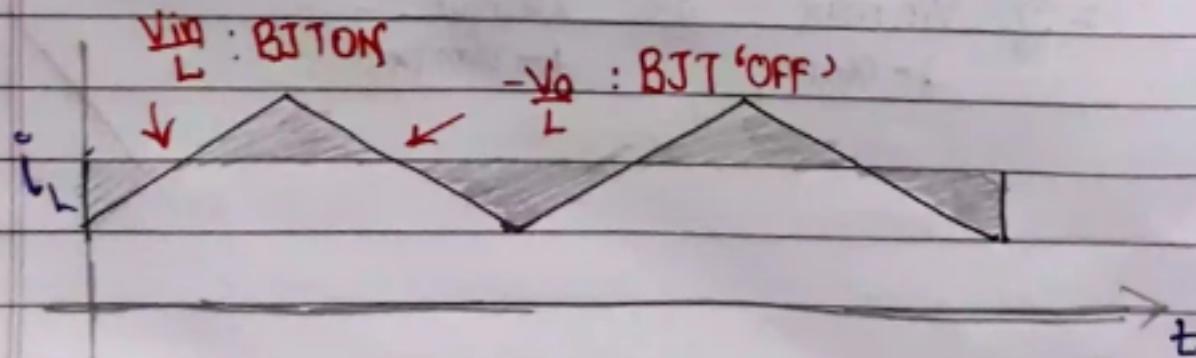$V_{in} \rightarrow$ BJT on, $-V_o \rightarrow$ Diode conducting
 Diode withstandin cap :- $V_{in} + V_o$. (max rating)




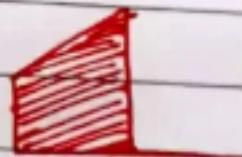

- Current thr. BJT

Avg value: I_{in} .

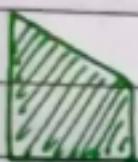Peak: $I_{in} + I_{o} + \frac{\Delta I_L}{2}$



- Current thr. the diode

Avg:- I_o

Rating:- Peak:- $I_{in} + I_o + \frac{\Delta I_L}{2}$

The value & so of L is same as boost converter i.e.

$C = I_o \cdot d$

$\Delta V \cdot f_s$

⇒ IMP FORMULAE & EQNs

V_{in} = Input voltage

V_{out} = Output voltage.

I_{out} = Output load current

$V_{in\ (max)}$ = Max input voltage

$V_{in\ (min)}$ = Min input voltage.

ΔI_L = Peak to peak inductor / output current ripple

ΔV_{out} = Output peak-to-peak voltage ripple.

L = Inductance (Filter)

C = Capacitance (Filter)

→ BUCK:

1. $D_{min} = \text{Min Duty cycle}$

$\eta = \text{Efficiency} = 0.9 \dots \text{assume}$

$$D_{min} = \frac{V_{out}}{V_{in(max)}} \times \eta$$

2. $\Delta I_L = 0.1 \times I_{out}$

$$L = \frac{V_{out} (V_{in(max)} - V_{out})}{\Delta I_L \times f_s \times V_{in(max)}} , f_s = \text{Switching frequency (Hz)}$$

$$\Delta I_L = 10\% \text{ of } I_{out} \geq 0.1 \cdot I_{out}$$

3. $\Delta V_{out} = \text{or } 2\% \text{ of } V_{out}$

$$= 0.02 \cdot V_{out}$$

$$C_{out(min)} = \frac{\Delta I_L}{8 \cdot f_s \times \Delta V_{out}}$$

4. $D_{min} = \frac{V_{out}}{V_{in(max)}} - \text{Min value of } D \text{ when } V_{in(max)}$

$D_{max} = \frac{V_{out}}{V_{in(min)}} - \text{Max value of } D \text{ when } V_{in(min)}$

→ BOOST:

$$1. \frac{V_{out}}{V_{in}} = \frac{I_{in}}{I_{out}} = \frac{1}{1-D}$$

$$D = 1 - \frac{V_{in(min)}}{V_{out}} \times \eta$$

$$\Delta I_L = 10\% \times I_{out} \times \frac{V_{out}}{V_{in}} \dots \text{Induct current ripple.}$$

$$I_{SW(max)} = \frac{\Delta I_L}{2} + \frac{I_{out}}{1-D}$$

$$L = \frac{V_{in} \times (V_{out} - V_{in})}{\Delta I_L \times f_s \times V_{out}}$$

ΔV_{out} : Output voltage ripple

$$L_{out(\min)} = \frac{I_{out} \times D}{f_s \times \Delta V_{out}}$$

→ Buck-Boost

$$1. \frac{V_o}{V_{in}} = \frac{-D}{1-D}, \quad D_{\min} = \frac{V_o}{(V_o + V_{in(\max)})}$$

$$2. L = \frac{V_{in(\max)} \times D_{\min}}{\Delta I_L \times f_s}, \quad \Delta I_L: \text{current ripple}$$

$$3. D_{\max} = \frac{V_o}{V_{in(\min)} + V_o}$$

$$\therefore L_{out} = \frac{2 \times D_{\max}}{f_s \cdot \Delta V_{out}}, \quad \Delta V_{out} = 2 \times V_{out} \\ = 0.02 \times V_{out}$$