

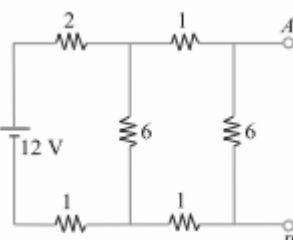
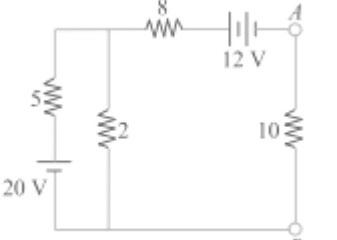
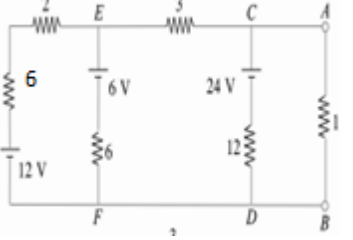
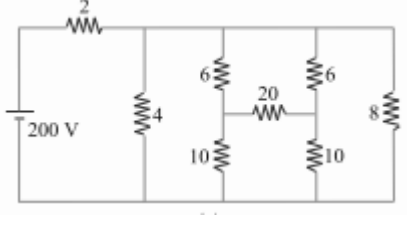
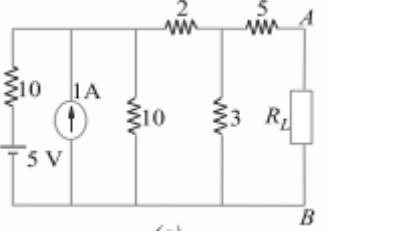
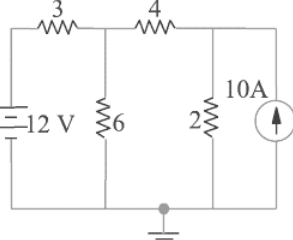
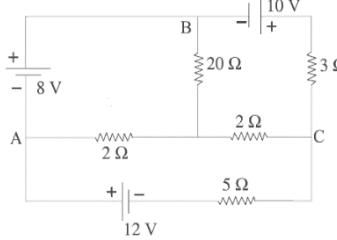
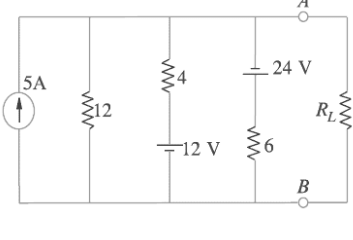


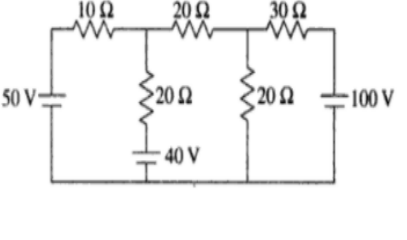

Bharatiya Vidya Bhavan's
Sardar Patel Institute of Technology
 Bhavan's Campus, Munshi Nagar, Andheri (West), Mumbai-400058-India
 (Autonomous College Affiliated to University of Mumbai)










Applied Science and Humanities Department

Batch X1	<p>1. Calculate current supplied by Thevenin's equivalent voltage</p> 	<p>2. Find $I_{10\Omega}$ using Thevenin's theorem</p> 	<p>3. Calculate current through 1Ω using Norton's Theorem.</p> 	<p>4. Calculate $I_{8\Omega}$ using Norton's Theorem.</p> 	<p>5. Calculate value of maximum power transferred by the circuit.</p> 
Batch X2	<p>1. Find current through 4Ω resistor using Thevenin's Theorem</p> 	<p>2. Calculate current through 5Ω resistance using Thevenin's Theorem</p> 	<p>3. Calculate current through R_L using Norton's Theorem</p> 	<p>4. Calculate $I_{10\Omega}$ using Norton's theorem</p> 	<p>5. Calculate value of maximum power transferred by the circuit.</p> 

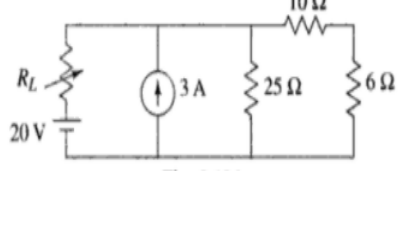

Bharatiya Vidya Bhavan's
Sardar Patel Institute of Technology
 Bhavan's Campus, Munshi Nagar, Andheri (West), Mumbai-400058-India
 (Autonomous College Affiliated to University of Mumbai)

Applied Science and Humanities Department

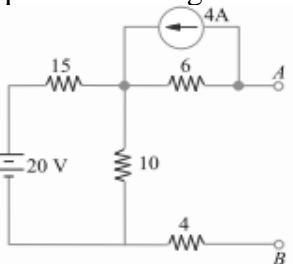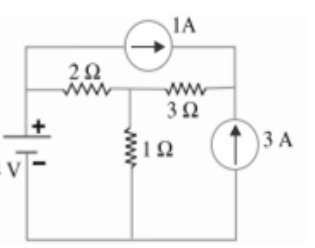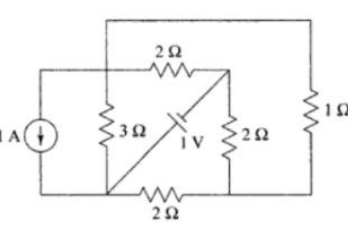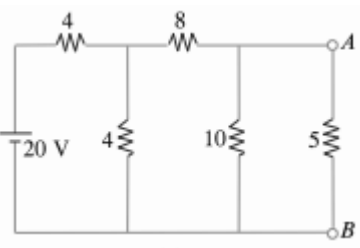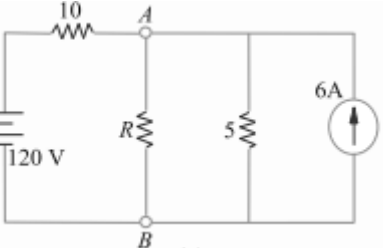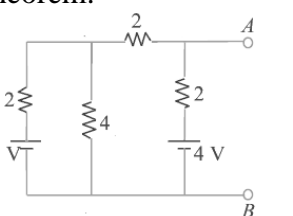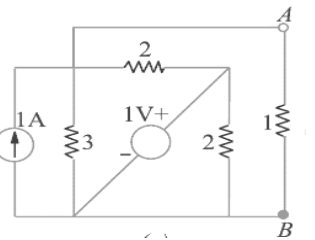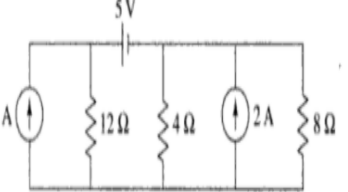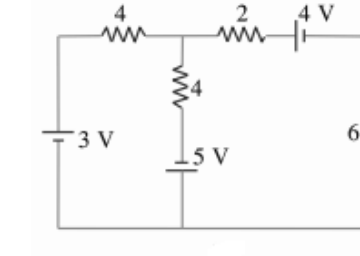Batch X3	<p>1. Calculate current supplied by Thevenin's equivalent voltage</p> 	<p>2. Find $I_{1\Omega}$ using Thevenin's theorem</p> 	<p>3. Calculate current flowing through 1Ω using Norton's Theorem</p> 	<p>4. Calculate $I_{5\Omega}$ using Norton's Theorem.</p> 	<p>5. Calculate value of maximum power absorb by R.</p> 
Batch X4	<p>1. Calculate current flowing through $R_L=2\Omega$ connected between A & B using Thevenin's theorem.</p> 	<p>2. Calculate current flowing through 1Ω using Thevenin's theorem</p> 	<p>3. Calculate current through 8Ω using Norton's Theorem</p> 	<p>4. Calculate current through 6Ω using Norton's Theorem</p> 	<p>5. Calculate value of maximum power transferred by the circuit.</p> 